

Unattractive because the peaky nature of IC adds many harmonics to the supply current.


(ii) Suitable model is

$$I = C \frac{dv}{dt} = C \frac{V_R}{1/f_s}$$

$I_{pk} = \frac{V_p}{R_L}$  and is more or less constant at this value

$$\therefore \frac{V_p}{R_L} = C \frac{V_R}{1/f_s}$$

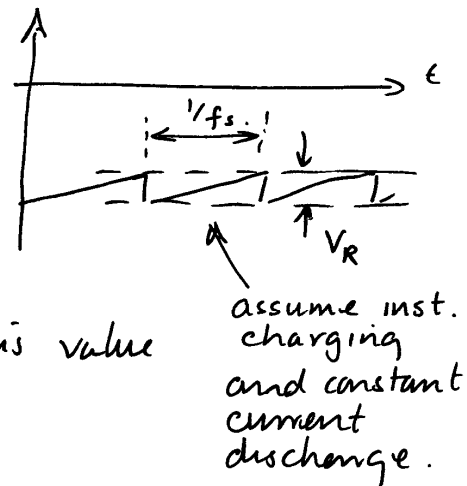
$$\text{or } C = \frac{V_p}{R_L V_R f_s} = \underline{2.8mF} \quad [0.7V \text{ diode drop has been neglected}]$$



(iii) Worst case condition

is minimum  $V_i$   
( $V_s \sqrt{2} - V_R$ )


and maximum  $I_L$

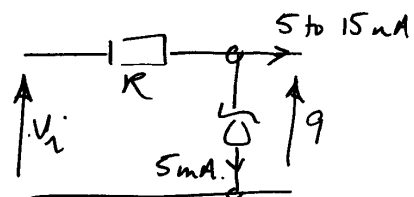

$$\therefore R_{max} = \frac{V_s \sqrt{2} - V_R - 9}{15mA + 5mA} = \frac{28.3 - 2 - 9}{20mA} = \underline{865\Omega}$$

The 0.7V diode drop has been neglected.

(iv) ripple equivalent circuit.....

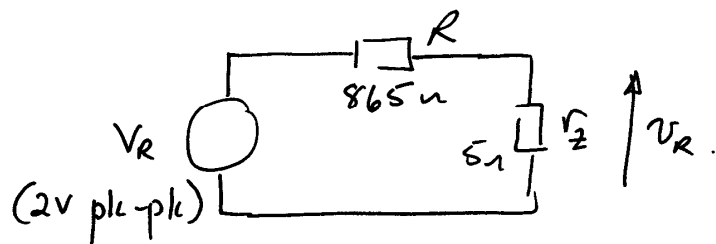


$$V_R = 2 \times \frac{5}{865 + 5} = \frac{10}{870} = \underline{\underline{11.5 \text{ mV}}}$$

(v) If output is short circuited to ground, all of  $V_{in}$  appears across  $R$ .

Assuming that  $V_{in} = V_{pk}$  (a worst case assumption from a power point of view)

$$P_R = \frac{V_p^2}{R} = \frac{(20\sqrt{2})^2}{865} = \frac{800}{865} = \underline{\underline{0.92 \text{ W}}}$$

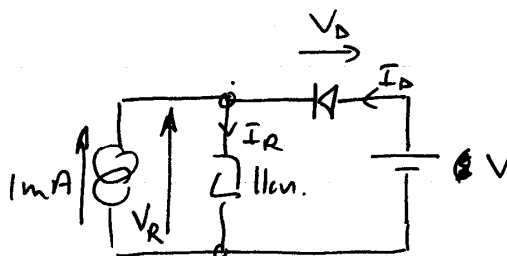Q2. (a) (i) On point of conduction,  $I_D = 0$ ,  $V_D = 0.7$



If  $I_D = 0$ , all of  $1 \text{ mA}$  goes through  $1 \text{ k}\Omega$  so  $V_R = 1 \text{ mA} \times 1 \text{ k}\Omega = 1 \text{ V}$ . Since  $V_R$  is on the diode cathode, diode anode will be  $V_R + 0.7 = V = \underline{\underline{1.7 \text{ V}}}$ .

(ii) If  $V = +5 \text{ V}$ , diode will conduct and  $V_R = V - 0.7 = 5 - 0.7 = 4.3$ .

So  $I_R = 4.3 \text{ mA}$ .  $1 \text{ mA}$  of this comes from the current source, the

rest comes from  $I_D$  since

$$I_D + 1\text{mA} = I_R$$

$$\text{so } I_D = 4.3\text{mA} - 1\text{mA} = \underline{\underline{3.3\text{mA}}}$$


$$V_D = \underline{\underline{0.7\text{V}}}$$

When  $V = -5\text{V}$ , diode cathode is at  $V_R$  volts which is  $1\text{mA} \times 1\text{k}\Omega = 1\text{V}$ . So diode is reverse biased and the reverse bias is

$$V_{D(RB)} = 1 - (-5) = \underline{\underline{6\text{V}}}$$

$$\text{and } I_D = \underline{\underline{0\text{mA}}}$$

(iii).

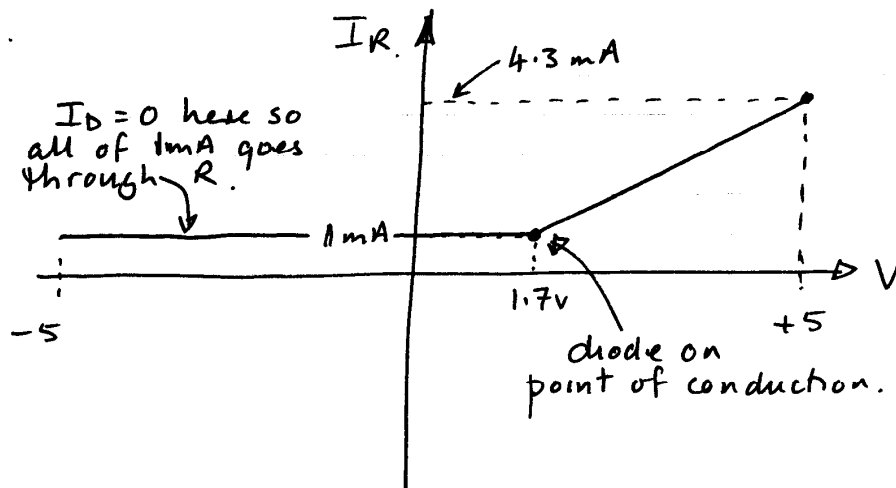


(b) (i) lead edge...

- initial voltage is zero
- aiming voltage  $10 \times \frac{R_2}{R_1 + R_2} = 6\text{V}$ .

$$V_x = 6(1 - e^{-t/\tau})$$


$$\text{where } \tau = 33\text{nF} \times 3\text{k}\Omega // 2\text{k}\Omega$$
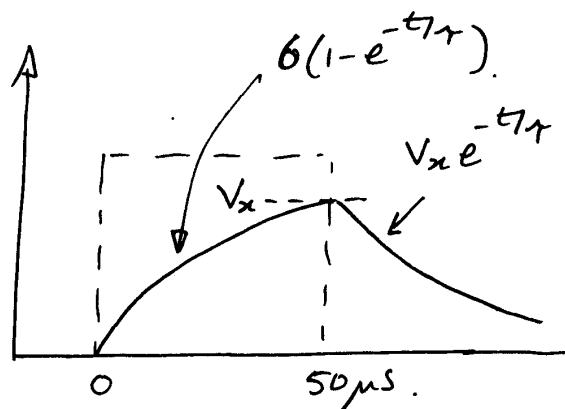
$$= 33\text{nF} \times 1.2\text{k}\Omega = 39.6\mu\text{s}.$$



$$V_x = 6(1 - e^{-50/39.6}) = \underline{\underline{4.3 \text{ V}}}$$

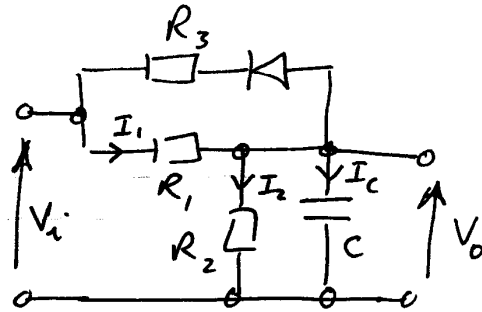
- (ii) On leading edge, C initially discharged so initial  $I_c = 10/R_1 = 5 \text{ mA}$ .



Since diode does not conduct in response to leading edge,  $V_x$  is the same as in part (i), i.e.  $4.3 \text{ V}$ . and  $\tau = 39.6 \mu\text{s}$  as before

On trailing edge,  $V_i$  goes to zero, but C is charged up to  $V_x$ . D conducts and sees the three resistors in parallel as a discharge path so  $I_p = -\frac{4.3}{R_1 \parallel R_2 \parallel R_3} = -\underline{\underline{5.73 \text{ mA}}}$ .
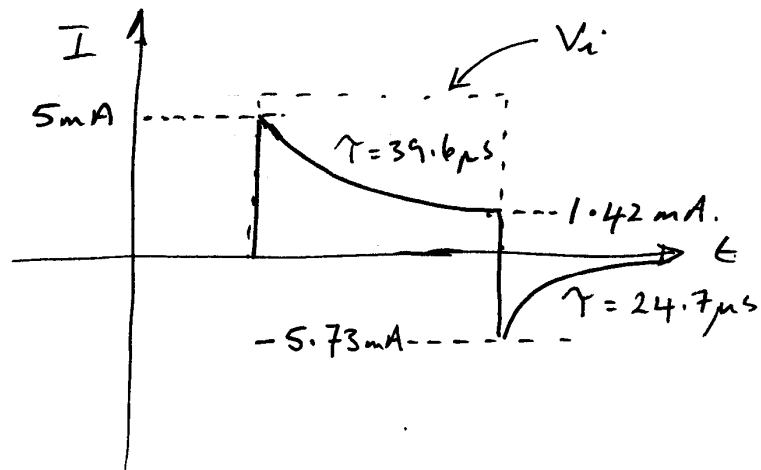
$$\text{and } \tau = 33 \text{ nF} \times R_1 \parallel R_2 \parallel R_3 = 33 \text{ nF} \times 750 \Omega = \underline{\underline{24.75 \mu\text{s}}}$$



At end of pulse  $I_c = I_1 - I_2$

$$= \frac{10 - 4.3}{2 \text{ k}\Omega} - \frac{4.3}{3 \text{ k}\Omega}$$

$$= (2.85 - 1.43) \text{ mA} = \underline{\underline{1.42 \text{ mA}}}$$

Q3 (a) (i) on state  $I_D = \frac{V_{cc}}{R_L}$ , neglecting  $r_{DS(on)}$


$$= \frac{42}{5} = \underline{\underline{8.4 \text{ A}}}$$

(ii) on state  $P_D \approx (8.4)^2 r_{DS(on)}$

$$= \underline{\underline{7.1 \text{ W}}}$$

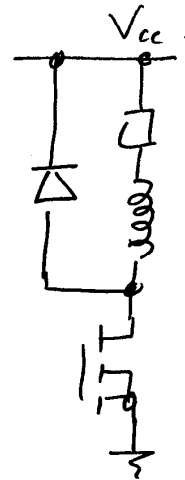(iii) An inductive load would store energy. This would not cause a problem on turn on but would give rise to a large transient voltage when the FET tried to switch off. Can be controlled by an idling diode as shown....

The diode provides a path for the inductor current when the switch turns off.



[Note that answers to pt (i) + (ii) will be slightly different from those given if  $r_{DS(on)}$  not neglected in part (i).]

(b) Two equations ...

$$V_{cc} = (I_F + I_C)R_L + I_F(R_1 + R_2) \quad \text{--- (1)}$$

$$\text{and } I_C R_E + 0.7 = I_F R_2 \quad \text{--- (2)}$$


$I_B$  is assumed to be negligible.

developing (1) ...

$$V_{cc} = I_C R_L + I_F(R_1 + R_2 + R_L) \quad \text{--- (3)}$$

developing (2) ...
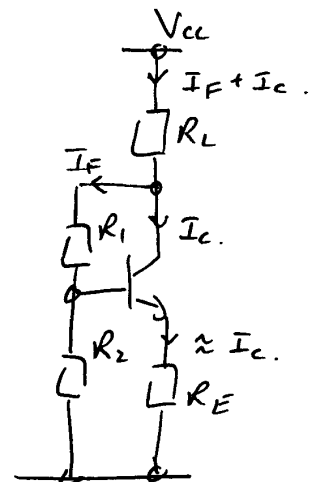
$$I_F = \frac{I_C R_E + 0.7}{R_2} \quad \text{--- (4)}$$



putting 4 into 3 ...

$$V_{CC} = I_C R_L + \frac{I_C R_E + 0.7}{R_2} (R_1 + R_2 + R_L)$$

$$V_{CC} - \frac{0.7(R_1 + R_2 + R_L)}{R_2} = I_C \left( R_L + \frac{R_E(R_1 + R_2 + R_L)}{R_2} \right)$$

$$18 - 2.24 = I_C (4.7k + 6.4k)$$

$$\frac{15.76}{11.1k\Omega} = I_C = \underline{1.42 \text{ mA}}$$

$$V_C = \text{So } I_F = \frac{1.42 \text{ mA} \times 2k\Omega + 0.7}{33k\Omega} = 107 \mu\text{A}$$

$$V_C = 18 - (1.42 \text{ mA} + 107 \mu\text{A}) 4.7k\Omega$$


$$= 18 - 7.18 = \underline{10.8 \text{ V}}$$


$$V_B = 1.42 \times 2k\Omega + 0.7 = \underline{3.54 \text{ V}}$$

(11)

$C_1 + C_4$  are coupling capacitors

$C_2 + C_3$  are decoupling capacitors.

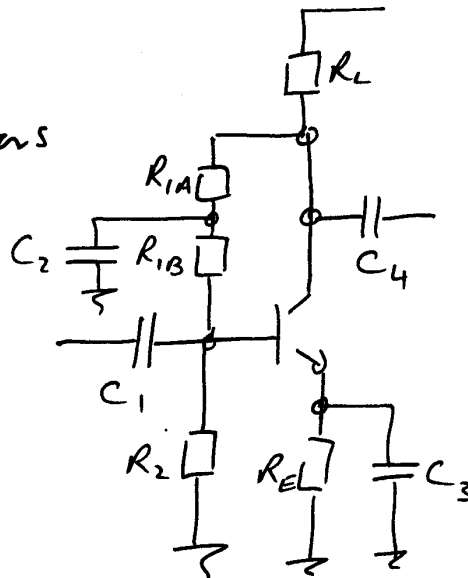

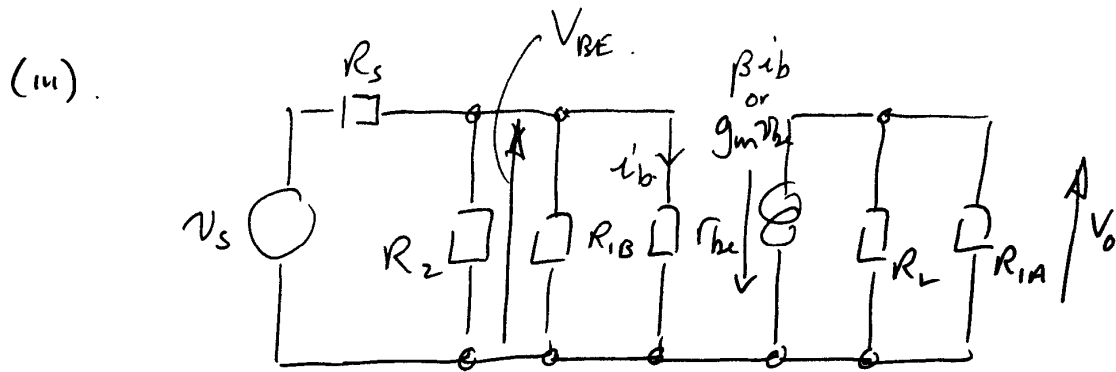


minus 1 mark per error.

Q4 (a) (i).  $\frac{V_o}{V_i} = -\frac{R_2}{R_1}$

suitable values would have a ratio of 10 with both resistors  $> 200\Omega$  and  $< 1\text{M}\Omega$ .

(ii)

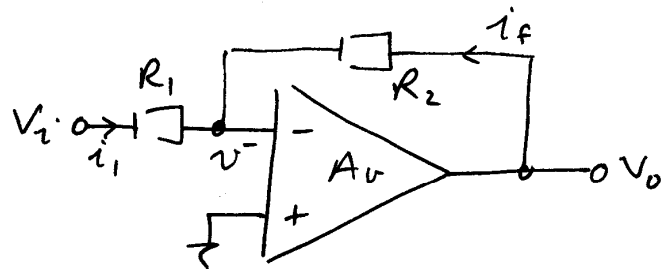

$$i_i + i_f = 0$$

$$\downarrow$$

$$\frac{v_i - v^-}{R_1} + \frac{v_o - v^-}{R_2} = 0$$

$$\frac{v_i}{R_1} + \frac{v_o}{R_2} = v^- \left[ \frac{1}{R_1} + \frac{1}{R_2} \right]$$

$$\text{or } v^- = \frac{v_i R_2}{R_1 + R_2} + \frac{v_o R_1}{R_1 + R_2}$$

$$\text{Also, } v_o = A_v (v^+ - v^-)$$

$$= A_v \left( 0 - \frac{v_i R_2}{R_1 + R_2} - \frac{v_o R_1}{R_1 + R_2} \right)$$

$$\text{so } v_o \left[ \frac{1}{A_v} + \frac{R_1}{R_1 + R_2} \right] = - \frac{v_i R_2}{R_1 + R_2}$$


$$\text{So } \frac{V_o}{V_i} = - \frac{R_2 / (R_1 + R_2)}{\left[ \frac{1}{A_v} + \frac{R_1}{(R_1 + R_2)} \right]}$$

(b) (i)

$$v^+ = V_i \frac{R_2}{R_1 + R_2}$$

$$V_o = v^+ \frac{R_F + R_3 \parallel R_4}{R_3 \parallel R_4}$$
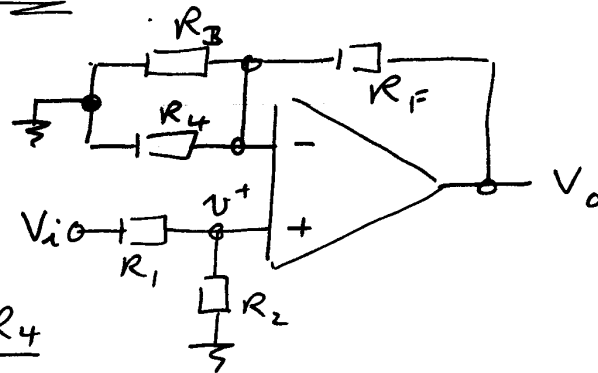
$$\therefore \frac{V_o}{V_i} = \frac{R_2}{R_1 + R_2} \cdot \frac{R_F + R_3 \parallel R_4}{R_3 \parallel R_4} = 0.4 \cdot \frac{11}{1} = \underline{\underline{4.4}}$$



(ii) The same except that  $R_1$  becomes  $R_2$  and vice versa

$$\frac{V_o}{V_i} = \frac{R_1}{R_1 + R_2} \cdot 11 = 0.6 \cdot \frac{11}{1} = \underline{\underline{6.6}}$$

(iii) When  $V_1 + V_2 = 0$ ,  $v^+ = 0$

$$\frac{V_o}{V_i} = - \frac{R_F}{R_3} = - \frac{10k}{1.5k} = - \underline{\underline{6.66}}$$

(iv) The same as (iii) except  $R_3$  becomes  $R_4$  + vice versa.

$$\frac{V_o}{V_i} = - \frac{R_F}{R_4} = - \frac{10k}{3k} = - \underline{\underline{3.33}}$$

[note that in cases (iii) + (iv), there is no voltage across the resistor connected to 0V so it doesn't affect gain]



$$(v) \quad V_1 = 3V, \quad V_2 = 25 \sin \omega t, \quad V_3 = a + b \sin \omega t \\ \text{and } V_4 = 5 - 3 \sin \omega t$$

$$\frac{V_0}{V_1} \times V_1 + \frac{V_0}{V_2} \times V_2 + \frac{V_0}{V_3} \times V_3 + \frac{V_0}{V_4} \times V_4 = 0.$$

$$13.2 + 13.2 \sin \omega t + (-6.67a - 6.67b \sin \omega t) \\ + (-3.33.5 + 3.33.3 \sin \omega t) = 0.$$

$$\text{dc terms } 13.2 - 6.67a - 16.65 = 0.$$

$$\text{or } -a = \frac{16.65 - 13.2}{6.67} = 517 \text{ mV}.$$

$$\therefore a = \underline{\underline{-517 \text{ mV}}}.$$

$$\text{ac terms } 13.2 - 6.67b + 9.99 = 0.$$

$$\text{or } b = \frac{13.2 + 9.99}{6.67} = \underline{\underline{3.48}}.$$