
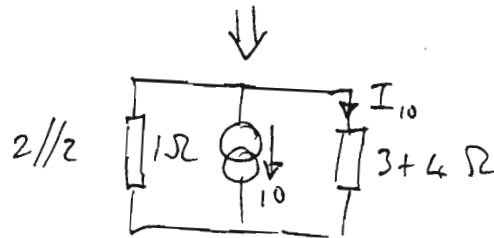


Solutions

- 1 (a) The response of a linear circuit to several sources acting together is equal to the algebraic sum of the responses due to each source acting individually.

2

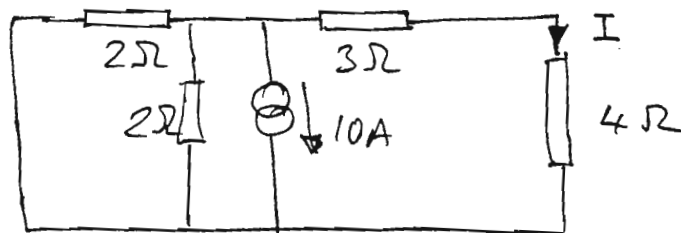
- (b) 10 A source alone (s/c voltage source)



$$I_{10A} = \frac{1}{1+7} \times 8 = \frac{10}{8} = -1.25A \quad (\text{opposite direction to that shown}).$$

2

- 4 V source alone (o/c current source)

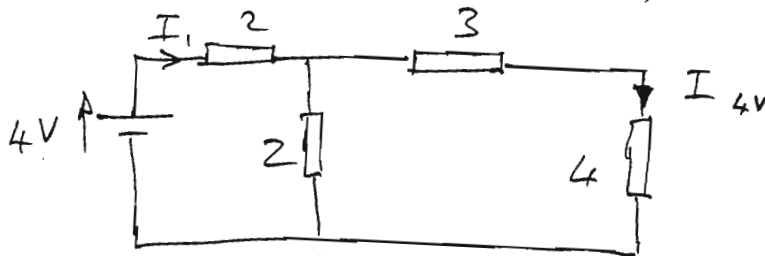

$$I_1 = \frac{4}{2+2//7} = \frac{4}{2+1.555} = 1.125A$$


$$I_{4V} = \frac{2}{9} \times 1.125 = 0.25A$$

2

$$\therefore I = I_{10A} + I_{4V} = -1.25 + 0.25 = -1A$$


2

Q1 (cont.)

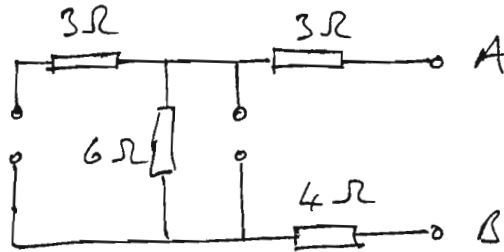(c) To get R_T o/c current sources

4


$$R_T = 3 + 6 + 4 = 13 \Omega$$

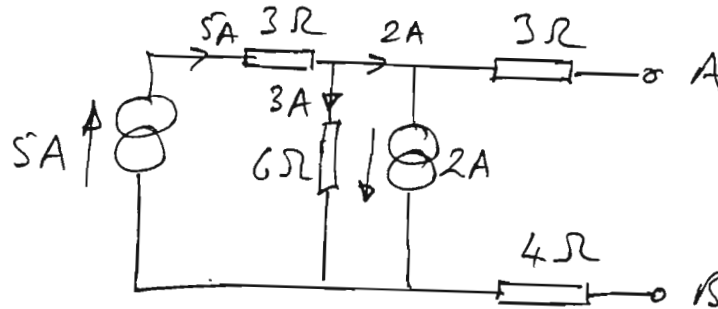For E_T 

$$V_{6\Omega} = 3 \times 6 = 18 \text{ V} \equiv \text{voltage across } AB$$

hence $E_T = 18 \text{ V}$.

4

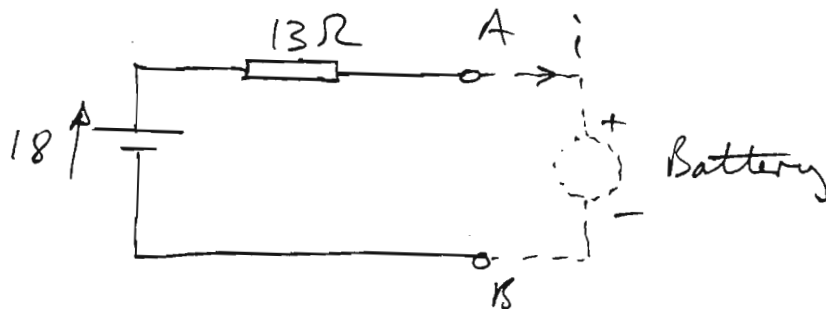

Battery will always receive power since the supply voltage always exceeds the battery voltage.

When charged to 15V

$$\text{Current } i = \frac{18 - 15}{13} = \underline{0.23 \text{ A}} \quad 2$$

Q2 (a) Capacitor energy stored in electric field
Inductor energy stored in magnetic field. 2

Capacitor energy established by charging
 from a voltage source through a resistor. 2

Inductor energy established by setting up
a current through it.

Energy recovered by:-

Discharging capacitor through a resistor
 Removing source of current in the inductor 2
 and allow the current to dissipate through a
 resistive load.

(b) Instantaneous power $p = vi = L i \frac{di}{dt}$ 1

Energy absorbed in interval t

$$= \int_0^t p dt' = L \int_0^t i \frac{di}{dt'} dt' \quad 1$$

$$= L \int_0^I i di$$


where I is the
 current flowing at
 time t

$$= \underline{\underline{\frac{1}{2} L I^2}}$$

2

Q 2 (cont.)

(c)

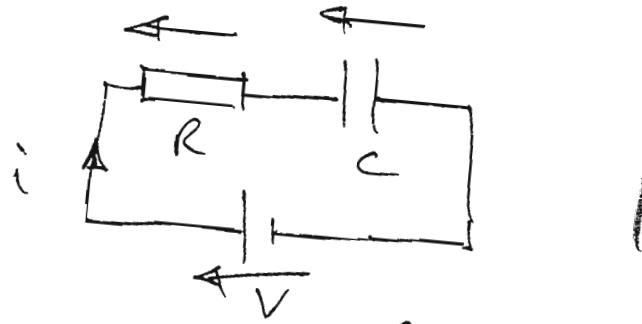

Apply K2

$$V - iR - \frac{1}{C} \int i dt = 0 \quad 1$$


$$\therefore -R \frac{di}{dt} = \frac{i}{C}$$

$$\therefore \int \frac{di}{i} = -\frac{1}{RC} \int dt$$

$$\therefore \ln i = -\frac{1}{RC} t + A \quad 1$$

$$\text{at } t=0 \quad i = \frac{V}{R} \quad \therefore A = \ln V/R \quad 1$$
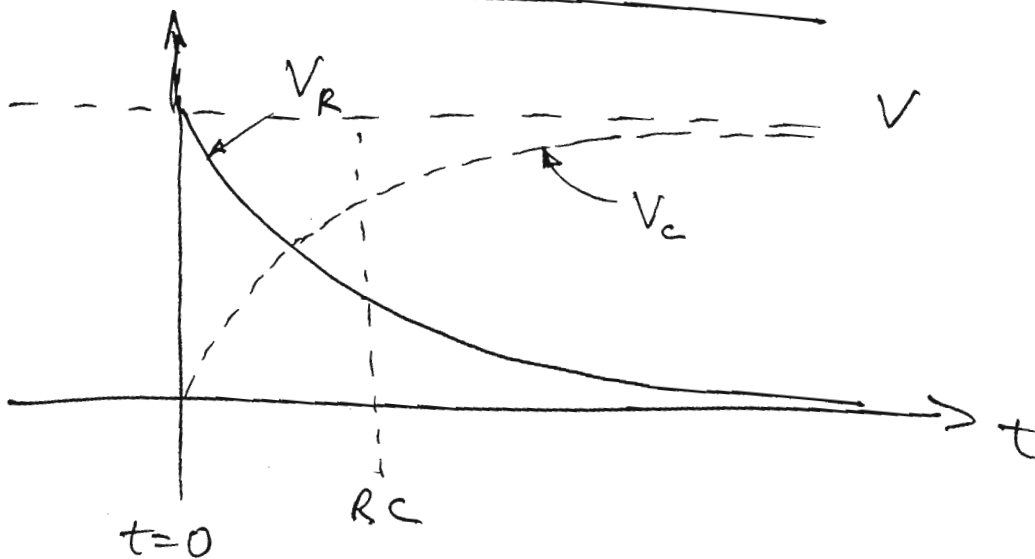
$$\therefore i = \frac{V}{R} e^{-t/RC} \quad 2$$




Q3 (a) Thevenin:- an active network having 2 accessible terminals, A and B, behaves, as far as the load is concerned, as if the network contained a single voltage source, E_T , and a series internal impedance, Z . (5)


$Z_T \equiv$ impedance across AB with current sources o/c and voltage sources s/c.

$E_T \equiv$ voltage across AB with load disconnected

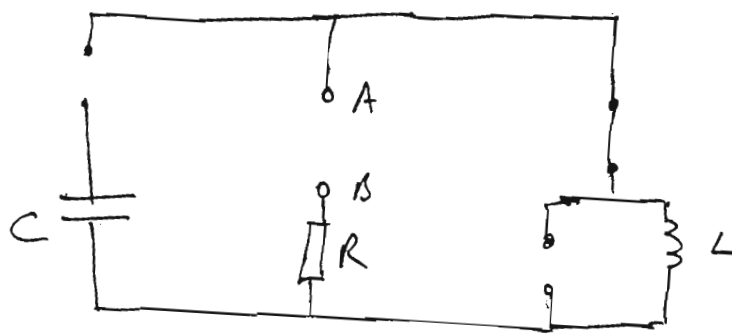(b) Z_T o/c current source, s/c voltage source



$$Z_T = R + j\omega L$$

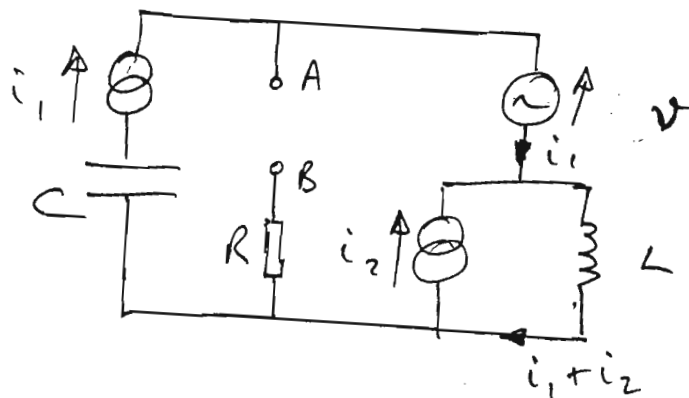


From inspection

$$E_T = v + j\omega L(i_1 + i_2)$$

Q3 (cont.)

⑥

(c)

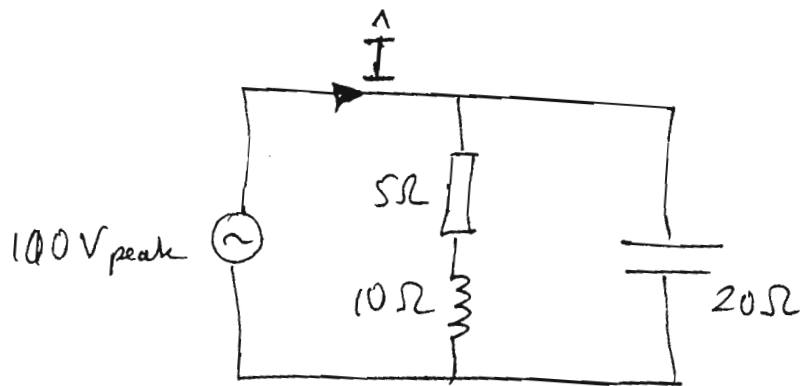

$$Z = (5 + j10) // -j20$$

$$= \frac{(5 + j10)(-j20)}{5 + j10 - j20} = \frac{(2 - j)100}{5 - j10}$$

rationalize

$$= \frac{100(2 - j)(5 + j10)}{5^2 + 10^2}$$


$$= \frac{100(10 - j5 + j20 + 10)}{125}$$

$$= \underline{16 + j12}$$

4

$$\hat{I} = \frac{100}{16 + j12} = \frac{100(16 - j12)}{16^2 + 12^2} = \underline{\underline{4 - j3}}$$

2

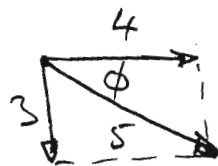Phase angle

$$|\hat{I}| = 5$$

$$\phi = \tan^{-1} 3/4 = \underline{\underline{-36.9^\circ}}$$


4

Q4 (a) Resonance occurs at a non-zero frequency where the imaginary part of the circuit is zero i.e. Z becomes real. 2

(b)

$$Z = j\omega L \parallel \left(R - \frac{j}{\omega c}\right)$$
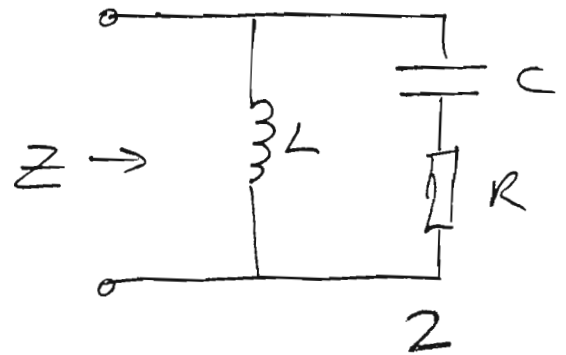
$$= \frac{j\omega L \left(R - \frac{j}{\omega c}\right)}{j\left(\omega L - \frac{1}{\omega c}\right) + R}$$



$$= \frac{j\omega L \left(R - \frac{j}{\omega c}\right) \left(R - j\left(\omega L - \frac{1}{\omega c}\right)\right)}{R^2 + \left(\omega L - \frac{1}{\omega c}\right)^2}$$

Numerator

$$= \left(j\omega L R + \frac{L}{c}\right) \left(R - j\left(\omega L - \frac{1}{\omega c}\right)\right)$$

$$= j\omega L R^2 + \frac{RL}{c} + \omega L R \left(\omega L - \frac{1}{\omega c}\right) - j \frac{L}{c} \left(\omega L - \frac{1}{\omega c}\right)$$

Imaginary part.

$$-\omega^2 L R^2 + \frac{L^2 \omega^2}{c} - \frac{L}{\omega c^2} = 0$$

$$\therefore \omega = \sqrt{\frac{L/c^2}{L^2/c - LR^2}}$$


$$= \sqrt{\frac{1}{LC - C^2 R^2}}$$

2

Q4 (cont.)

⑧

(c)

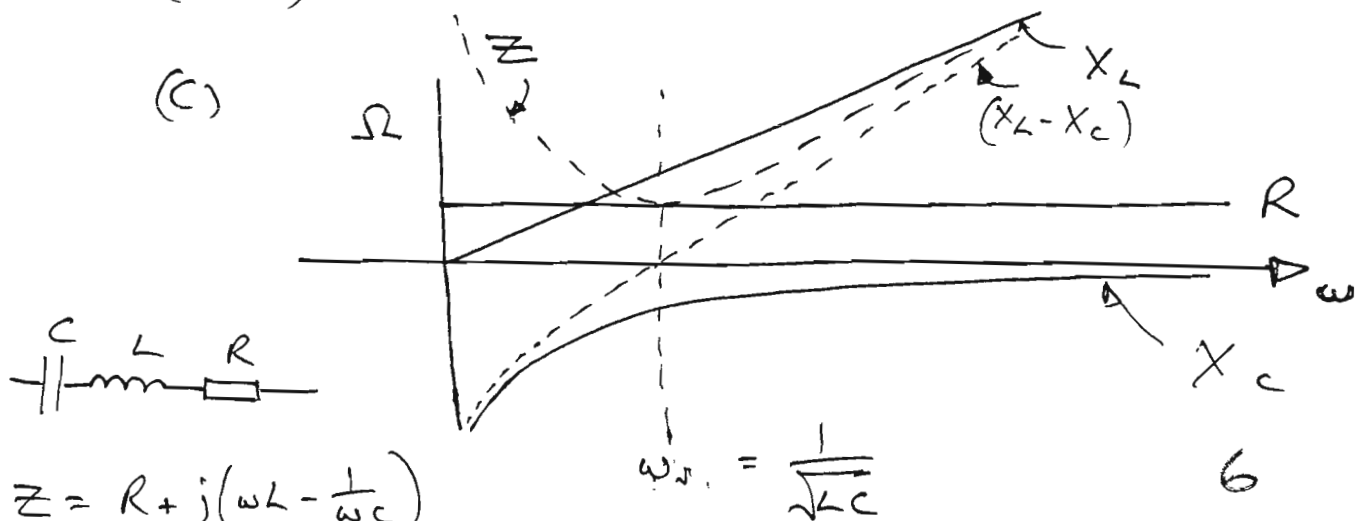

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$= R + (X_L - X_C)$$

(d) At resonance (30 kHz) $Z = R$

$$\therefore R = \frac{V}{I} = \frac{5}{20 \times 10^{-3}} = \underline{250 \Omega} \quad 2$$

now $Q = \frac{f_r}{\Delta f} = \frac{30}{3} = 10 = \frac{\omega_0 L}{R}$

$$\therefore L = \frac{10 \times 250}{2\pi \times 3 \times 10^4} = \underline{13.27 \text{ mH.}} \quad 2$$