

DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING

Spring Semester 2009 (30 minutes)

EEE 103 ANALOGUE CIRCUITS MID TERM TEST

Answer **ALL** questions. The numbers given after each section of a question indicate the relative weighting of that section.

REGISTRATION NUMBER:

WRITE YOUR ANSWERS ON THIS QUESTION PAPER

- 1 State the direction of conventional forward current flow (ie, "A to B" or "B to A") through the diode of figure 1. **{1 mark}**

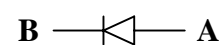


figure 1

Q1 Ans

- 2 In figure 2, D has a forward voltage drop of 0.7V. If $V_i = -4V$, will the diode be conducting? If the diode is conducting, what is its forward current? If the diode is not conducting, what is its reverse bias voltage? **{2 marks}**

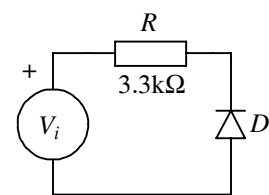


figure 2

Q2 Ans

- 3 In the circuit of figure 3 the diode has a forward voltage drop of 0.7V. At what value of V_i is the diode on the point of changing state from conducting to non-conducting? What is the value of I_D if (a), $V_i = 6V$? and (b), $V_i = -6V$? **{3 marks}**

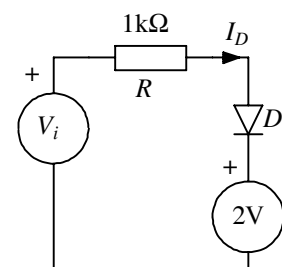


figure 3

Q3 Ans

- 4 In the circuit of figure 4, $R_1 = 2\text{k}\Omega$, $R_2 = 3\text{k}\Omega$ and $C = 1\mu\text{F}$ and V_i is shown in the **Q4** answer box. Evaluate the circuit time constant, τ , and values of V_O and I_C at $t = 0 + \delta t$ and at $t = 10\text{ms} + \delta t$ where δt is very small. Sketch the responses, V_O and I_C , of figure 4 on the axes given in the **Q4** answer box. **{9 marks}**


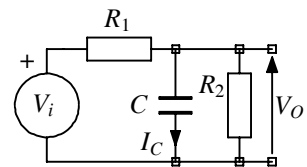


figure 4

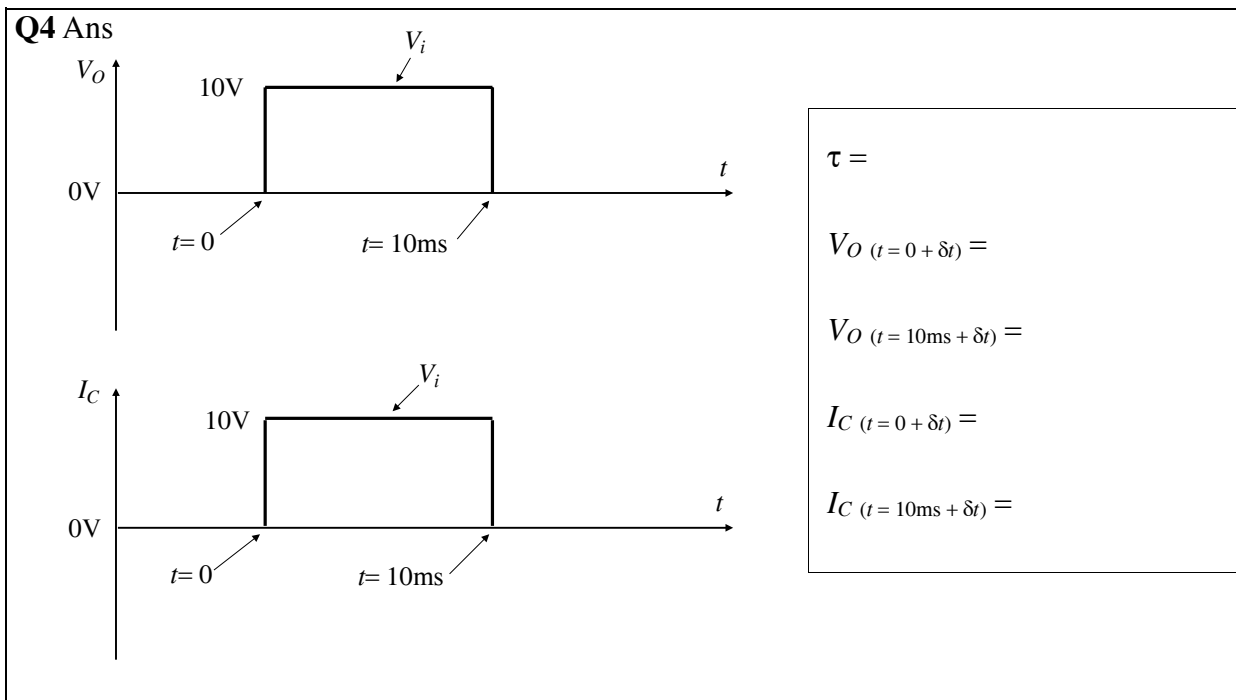

- 5 On the graph of V_i in the **Q5** answer box, sketch the response, V_O , of the circuit of figure 5 to the input voltage, V_i , shown. Label the magnitude of any step changes in V_O . Write down the circuit time constant. **{5 marks}**


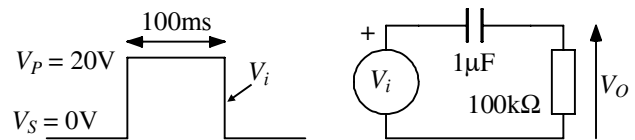


figure 5

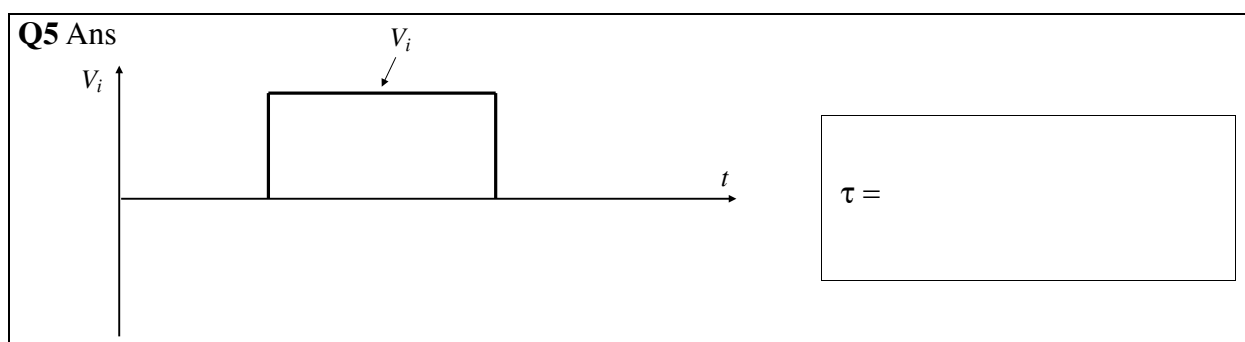

- 6 On the axes in the **Q6** answer box, sketch the waveshape you would expect to observe for a signal described by $V(t) = 4e^{-t/\tau} - 1$ for $t > 0$ and label all its important features. **{4 marks}**



- 7 The diode in figure 7 has a forward voltage drop of zero. On the axes in the **Q7** answer box, sketch the response of the circuit of figure 7 to the input pulse shown. Write down the rising and falling edge time constants in the boxes provided. **{3 marks}**


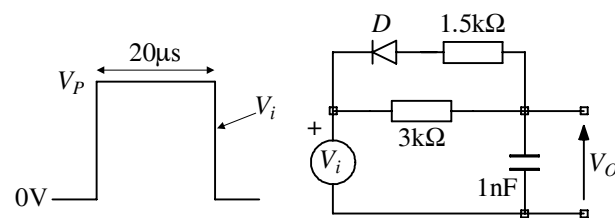


figure 7

Q7 Ans

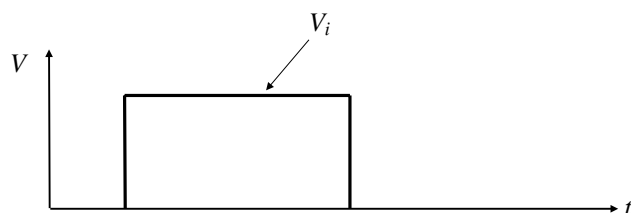

rising edge time constant =

falling edge time constant =

- 8 In figure 8 there are 5 circuit shapes that you have come across. In the **Q8** answer box, associate each circuit with the appropriate name from the following list;

half wave rectifier, clipping circuit, clamping circuit, zener diode regulator, full wave rectifier, voltage doubler, peak detector. **{5 marks}**

Q8 Ans

circuit (a) is a
circuit (b) is a
circuit (c) is a
circuit (d) is a
circuit (e) is a

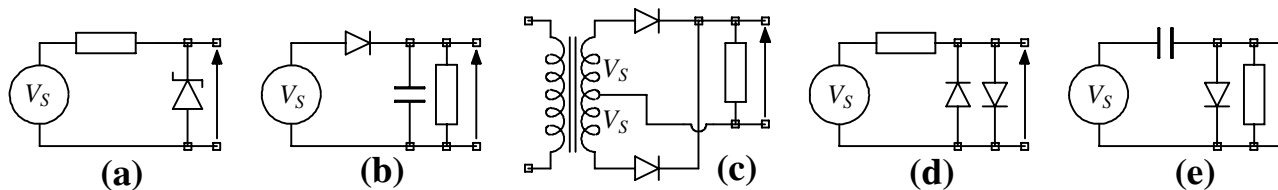


Figure 8

- 9 If V_S in the circuits of figure 8 is a 10V peak 50 Hz sinusoid, the diodes have a forward bias voltage drop of 0.7V and you can assume where necessary that the resistor is large, what is

- (i) the most negative voltage at the output of circuit (e)?
(ii) the range of voltage that can appear at the output of circuit (d)?
(iii) the waveshape you would expect to see at the output of circuit (c)? (You need to draw axes and label peak values and times.)
(iv) the most positive voltage at the output of circuit (b)? **{6 marks in total}**

Q9(i) Ans

Q9(ii) Ans

Q9(iii) Ans

Q9(iv) Ans