



The
University
Of
Sheffield.

Data Provided: Log 3 cycle x linear graph paper.

DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING

Spring Semester 2011-12 (2.0 hours)

EEE112 Engineering Applications

This paper comprises **TWO** sections, **A** and **B**. You may gain up to **60 MARKS** from **SECTION A** and **40 MARKS** from **SECTION B**. Attempt **ALL** the questions in **SECTION A**. Marks will be awarded for your best **TWO** solutions in **SECTION B**. Trial answers will be ignored if they are clearly crossed out. A formula sheet is included at the end of the exam paper. **The numbers given after each section of a question indicate the relative weighting of that section.**

SECTION A

1. a. Convert the following:

- i) 150° into radians,
- ii) -135° into radians,
- iii) $\pi/3$ radians into degrees,
- iv) $-3\pi/2$ radians into degrees,
- v) 2 radians into degrees.

(5)

b. A time varying current is described by the equation:

$$i(t) = -20 \cos\left(120\pi t + \frac{\pi}{2}\right) \text{ Amp. s}$$

For this equations write down:

- i) the amplitude,
- ii) the peak-to-peak current,
- iii) the frequency (NOT the angular frequency).
- iv) the period,
- v) the phase shift.

(5)

2. a. Solve the following simultaneous equations using the method of substitution (NOT by Cramer's Rule and NOT by Gaussian elimination) to find the values of x , y & z .

$$2x + 3y = 6$$

$$-2x + 3z = 0$$

$$x + 2y + 3z = -1$$

(3)

b.

- i) For the circuit shown in Figure 1 below, use loop current analysis (by defining closed current loops using Kirchhoff's Voltage law) to form 3 equations with 3 unknowns (where the unknowns are the currents I_1 , I_2 and I_3).
- ii) Using Cramer's Rule only (not Gaussian Elimination) solve the simultaneous equations found in part i) to find the values of the currents I_1 , I_2 and I_3 .

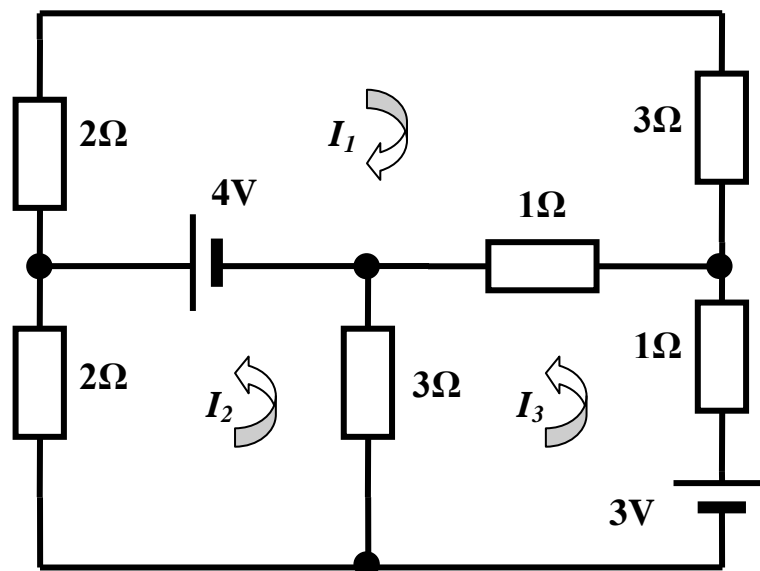


Figure 1

(11)

3. a. i) Find an expression to represent $5 \cos(\omega t) - 3 \sin(\omega t)$ in the form $R \sin(\omega t + \alpha)$ representing α in radians.
- ii) Find an expression to represent $-4.2 \sin(\omega t) - 3.1 \cos(\omega t)$ in the form $R \cos(\omega t + \alpha)$ representing α in radians

(6)

- b. A circuit has a voltage across its terminals of $v(t) = 5 \sin(\omega t)$ Volts and a current flowing through it of $i(t) = 10 \sin\left(\omega t - \frac{\pi}{2}\right)$ Amp.s. Therefore power (as a function of time) in this circuit can be found from the following equation:

$$P(t) = v(t) \cdot i(t) = 5 \sin(\omega t) \cdot 10 \sin\left(\omega t - \frac{\pi}{2}\right) \text{ Watts}$$

Using trigonometric identities, show that instantaneous power (as a function of time) in this circuit can also be represented by the equation:

$$P(t) = -25 \sin(2\omega t) \text{ Watts}$$

(4)

4. a. A current of $i(t) = 17 \sin(120\pi t - \frac{5\pi}{6})$ mAmp.s passes through each of the following components. Determine the voltage across each component as a function of time.

- i) A resistor of **1.2 kΩ**
- ii) A capacitor of **3 μF**
- iii) An inductor of **4 H**

(6)

- b. A voltage supply of $v(t) = 5 \sin(\omega t)$ Volts with a frequency of **900 kHz** is applied across a circuit consisting of a **47 kΩ** resistor connected in **parallel** with a **2.7 pF** capacitor.

- i) Calculate the current (as a function of time) that flows in the resistor.
- ii) Calculate the current (as a function of time) that flows in the capacitor.
- iii) Draw a Phasor Diagram showing the relationship between all the currents calculated in parts i) and ii) and the voltage, all on the same diagram.
- iv) Calculate the total current taken from the supply.

(12)

5. a. The general formula for a voltage decaying exponentially towards zero is:

$$v = E \cdot e^{-\frac{t}{\tau}}$$

where v is the voltage at time t , E is the voltage at time $t = 0$ and τ is the time constant. As t approaches infinity ($t \rightarrow \infty$) v approaches 0. Rearrange this equation to make t to be the subject.

(2)

- b. For the formula given in part a. above let $E = 12$ Volts and $\tau = 5$ mS. Find the value of t when $v = 1.6$ Volts.

(2)

- c. Consider a voltage decaying exponentially, with a time constant $\tau = 20$ mS, starting at $E = +10$ Volts and as t approaches infinity ($t \rightarrow \infty$) v approaches **-5 Volts**. Find the value of v when $t = 25$ mS.

(4)

SECTION B

6. a. Write down the general expression representing the **mean** of voltage function $v(t)$.

(2)

- b. A repeating voltage waveform with a period =10 seconds is shown in Figure 2 below:

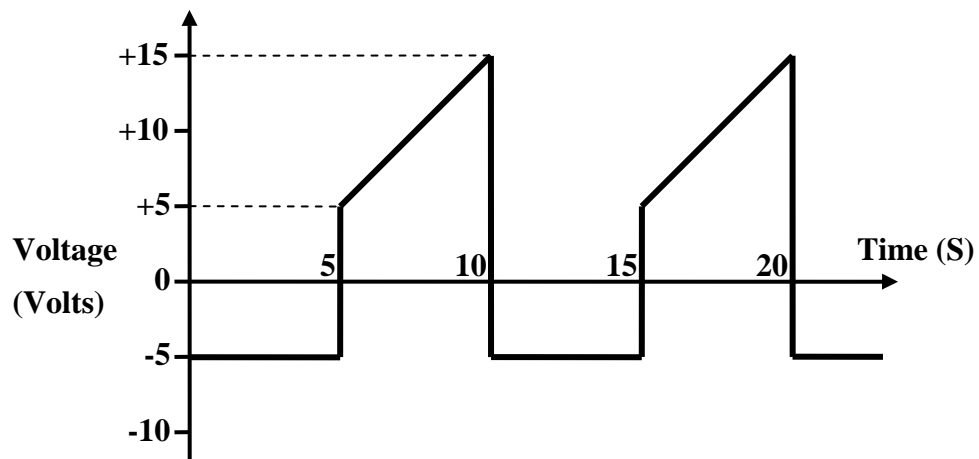


Figure 2

Write down equations to describe this voltage waveform, over one period, as a function of time. (*Hint: write down one function for the period 0 to 5 seconds and another for the period 5 to 10 seconds*). Next, using these equations, find the **mean** voltage of this waveform.

(10)

- c. Find the **Root Mean Squared** voltage for the waveform shown in part b. Figure 2 above.

(8)

7. a. Plot the following complex number points, all on the same **ARGAND** diagram:

- i) $2 + j3$
- ii) $j(2 + j4)$

(2)

- b. Convert the following:

- i) $-3 + j6$ into polar ($r\angle\theta$) form.
- ii) $5\angle -127^\circ$ into rectangular, also called Cartesian, form ($Re+jIm$).

(2)

- c. The following two impedances (Z) each consist of two components connected in series. One component in each case is a **resistor** the other is a **reactance** (either an **inductor** or a **capacitor**). Determine the value of both components for each of the following two impedances. Assume a frequency of 100 Hz.

- i) $Z = (70 + j200)\ \Omega$
- ii) $Z = 64\angle -39^\circ\ \Omega$

(6)

- d.

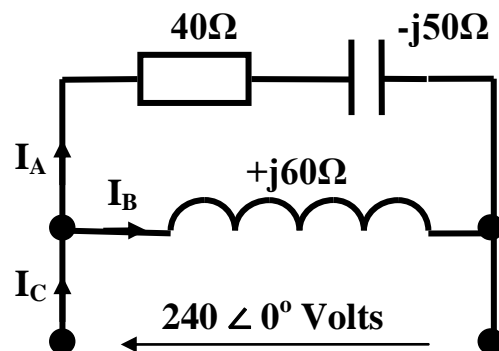


Figure 3

For the circuit shown in Figure 3 above:

- i) Find currents I_A and I_B .
- ii) Next find total current I_C .
- iii) Finally find the total impedance for the whole network.

(10)

8. a. Simplify the following equation: $3 \log(x) = \log(x^2)$ (2)
- b. i) An amplifier has a **voltage gain** of +40 dB. If $V_{in} = 4$ Volts then find V_{out} .
 ii) An attenuator has a **power gain** of -6 dB. If $P_{out} = 3$ Watts then find power P_{in} . (4)
- c. The current I_D flowing across the forward-biased **P-N** junction of a diode can be described by the equation:

$$I_D = I_s e^{\frac{V_D}{k}}$$

where I_s and k are **constants** and V_D is the voltage across the junction.

An engineer performs an experiment using a particular diode and taking a number of measurements of I_D and V_D . The values measured are shown in the Table 1 below:

| $I_D (mAmps)$ | $V_D (Volts)$ |
|---------------|---------------|
| 1 | 0.53 |
| 5 | 0.57 |
| 10 | 0.59 |
| 20 | 0.61 |
| 100 | 0.65 |
| 500 | 0.69 |
| 1000 | 0.71 |

Table 1

By plotting the data in Table 1 on 3-cycle Log-Linear graph paper provided show that the behaviour of the diode is consistent with an equation of the form given above. (7)

- d. Using the data in Table 1 above, find the values of the **constants** I_s and k . (7)

9. a. Given the differential equation:

$$5 \frac{dy}{dx} + 2x = 3$$

i) Find the **general solution**.

ii) Find the **particular solution** given $y = 1\frac{2}{5}$ when $x = 2$.

(5)

- b. Given the differential equation:

$$\frac{dy}{dx} = 9x^2y$$

Find the general solution and express your answer beginning $y =$

(5)

- c. Consider the circuit shown in figure 4 below:

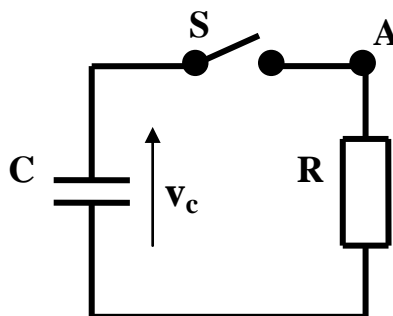


Figure 4

Assume that just before time $t = 0$ capacitor C has been charged so that its terminal voltage v_c is **10 Volts**. At time $t = 0$ switch S is closed and capacitor C discharges through resistor R . Using **Krichoff's current law** we can write the following differential equation describing the currents entering and leaving node A :

$$C \frac{dv_c}{dt} = -\frac{v_c}{R}$$

Solve the equation above and use the initial conditions given ($v_c = 10$ Volts at $t = 0$) to show that an equation for v_c can be written in the form shown below:

$$v_c = 10 e^{-\frac{t}{RC}} \quad (6)$$

- d. For the circuit described in part c. above and given $R = 2 \text{ k}\Omega$ and $C = 25 \text{ }\mu\text{F}$, find the value of t when v_c has fallen to **67 mVolts**.

(4)

FORMULA SHEET**Trig. Identities**

$$\sin(A + B) = \sin A \cos B + \cos A \sin B$$

$$\cos(A + B) = \cos A \cos B - \sin A \sin B$$

$$\sin(A - B) = \sin A \cos B - \cos A \sin B$$

$$\cos(A - B) = \cos A \cos B + \sin A \sin B$$

$$2 \sin A \cos B = \sin(A + B) + \sin(A - B)$$

$$2 \cos A \cos B = \cos(A - B) + \cos(A + B)$$

$$2 \sin A \sin B = \cos(A - B) - \cos(A + B)$$

$$\sin^2 \theta = \frac{1}{2}(1 - \cos 2\theta)$$

$$\cos^2 \theta = \frac{1}{2}(1 + \cos 2\theta)$$

Logarithmic Laws

$$\log_a x^n = n \log_a x$$

$$\log_a xy = \log_a x + \log_a y$$

$$\log_a \left(\frac{x}{y} \right) = \log_a x - \log_a y$$

Integration for $f(x)$

$$\int \sin x = -\cos x + c$$

$$\int \sin k.x = -\frac{1}{k} \cos k.x + c$$

$$\int \cos x = \sin x + c$$


$$\int \cos k.x = \frac{1}{k} \sin k.x + c$$

$$\int \frac{1}{x} = \ln(x) + c$$

PLJ

WRITE YOUR REGISTRATION NUMBER _____

Log 3 cycle x Linear

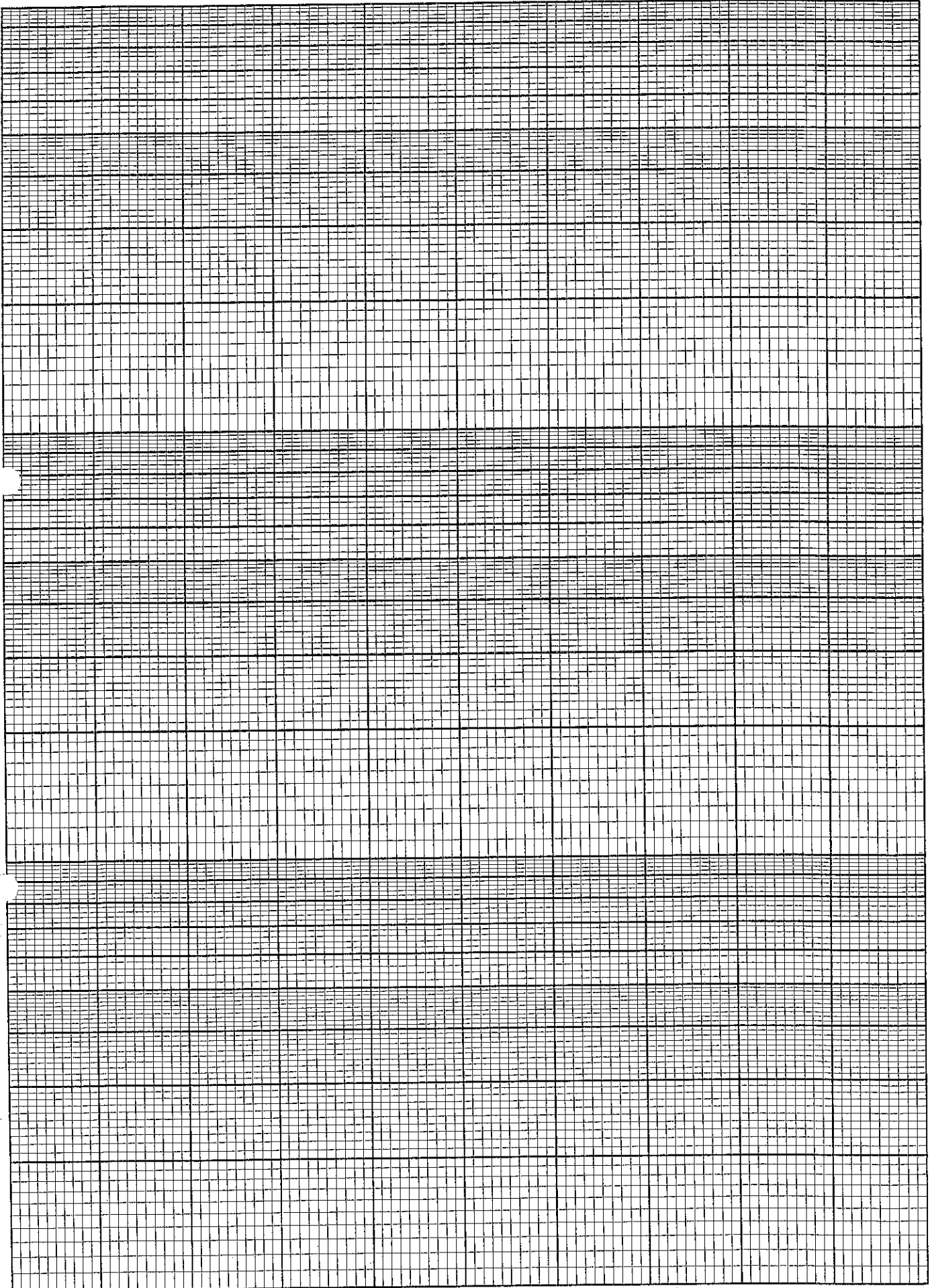

Return with Answer Book