

# Behavioural Models

- Continuous Assignment Statements
- Arithmetic Operators
- Decoders

# Continuous Assignment Statement

```
module AOI_5(output y_out, input a, b, c, d, e);  
    assign y_out = ~((a & b) | (c & d & e));  
endmodule
```

**assign** declares a continuous assignment. Whenever any of the variables on the RHS change (an event), the expression is re-evaluated to update the LHS. The assignment is ‘sensitive’ to the variables on the RHS.

```
module AOI_5(output y_out, input a, b, c, d, e, enable);  
    assign y_out = enable ? ~((a & b) | (c & d & e)) : 1'bz;  
endmodule
```

The conditional operator (**? :**) can be used to add an enable.

**`?`** lets you switch between the two expressions either side of **`:`**


If enable is asserted (true) the expression to the left of the colon is evaluated, otherwise the expression to the right of the **:** is evaluated.

# Concurrency

- A module may contain multiple continuous assignments
- Assignments are active concurrently with all other continuous assignments, primitives, instantiated modules, behavioral statements
- Continuous assignments can also be written without the **assign** keyword as part of a wire declaration
- Propagation (inertial) delay can be included in a continuous assignment

```
module AOI_5(output y_out, input a, b, c, d);  
  wire #1 y1 = a & b;  
  wire #1 y2 = c & d;  
  wire #1 y_out = ~(y1 | y2);  
endmodule
```



# Multiplexer with Continuous Assignment

 







```
module Mux_2_32 #(parameter word_size = 32) (  
    output [word_size - 1:0] mux_out;  
    input [word_size - 1:0] data_0, data_1;  
    input select  
);  
    assign mux_out = select ? data_1 : data_0  
endmodule
```

a parameter is a  
constant value  
defined within  
the module

Logic  
description

  

Verilog  
description

      

# 4-Bit Adder

- 4-bit adder adds two 4-bit binary inputs A and B, sets 4-bit output S
- Could describe structurally
  - Carry-ripple: 4 full-adders
- Behaviorally
  - Simply:  $S = A + B$
  - "always" procedure sensitive to A and B
    - Adder is combinational – must include all inputs in sensitivity list
    - Note: procedure resumes if *any* bit in either vector changes

```
module Add4(A, B, S);  
  
    input [3:0] A, B;  
    output [3:0] S;  
    reg [3:0] S;  
  
    always @(A, B) begin  
        S = A + B;  
    end  
endmodule
```

Built-in arithmetic operators include:

+ : addition

- : subtraction

\* : multiplication

/ : division

% : modulus

\*\* : power ("a \*\* b" is a raised to the power of b)

# 4-Bit Adder with Carry-In and Carry-Out

- Adders have carry-in and carry-out bits
- $S = A + B + C_i$ 
  - Yields correct sum
    - "+" operator handles different bit-widths – extends  $C_i$  to 4 bits, padded on left with 0s
  - But carry-out?
    - $S$  is only 4 bits;  $C_o$  is a fifth bit
- Solution – Do 5-bit add, separate fifth bit (carry-out) from lower four

```
module Add4wCarry(A, B, Ci, S, Co);  
  input [3:0] A, B;  
  input Ci;  
  output [3:0] S;  
  reg [3:0] S;  
  output Co;  
  reg Co;  
  reg [4:0] A5, B5, S5;  
  
  always @(A, B, Ci) begin  
    A5 = {1'b0, A};  
    B5 = {1'b0, B};  
    S5 = A5 + B5 + Ci;  
    S = S5[3:0];  
    Co = S5[4];  
  end  
endmodule
```

- Concatenation Operator "{ }" Joins bits from two or more expressions
- Expressions separated by commas within { }

alternative description :


```
always @(A, B, Ci) begin  
    {Co, S} = A + B + Ci;  
end  
endmodule
```

- Use concatenation on the left side of assignment
  - {Co, S} = A + B + Ci
  - Left side thus 5 bits wide
- Rule
  - For the + operator, all operands extended to width of widest operand, including left side
  - Left side is 5 bits → A, B, and Ci all extended to 5 bits, left padded with 0s
  - e.g., A: 0011, B: 0001, Ci: 0 → 00011+00001+00000 yields 00100
    - Co gets first 0, S gets 0100
- Though longer, previous description synthesizes to same circuit
  - reg [4:0] A5, B5, S5; – Synthesize into wires


 
# 4-bit Unsigned/Signed Magnitude Comparator

- Previously
  - Dealt only with unsigned numbers
    - input, output, reg declarations are unsigned unless otherwise specified
- Now consider a simple magnitude comparator that compares a 4-bit unsigned number A with a 4-bit signed number B, with outputs for greater than, less than, and equal
  - A can be 0 to 15 (0000 to 1111)
  - B can be -8 to 7 (1000 to 0111)
  - Need to represent both unsigned and signed numbers



Declare A input as before,  
but declare B input with  
**signed** keyword.  
When comparing A and B  
using "<", first convert  
unsigned A to signed  
value using **\$signed**  
system function.

```
module Comp4(A, B, Gt, Eq, Lt);  
  
    input [3:0] A;  
    input signed [3:0] B;  
    output Gt, Eq, Lt;  
    reg Gt, Eq, Lt;  
  
    always @(A, B) begin  
        if ($signed({1'b0,A}) < B) begin  
            Gt = 0; Eq = 0; Lt = 1;  
        end  
        else if ($signed({1'b0,A}) > B) begin  
            Gt = 1; Eq = 0; Lt = 0;  
        end  
        else begin  
            Gt = 0; Eq = 1; Lt = 0;  
        end  
    end  
endmodule
```

- "\$signed(A)" would not work – changes positive number to negative
  - e.g., 1000 would change from meaning 8 to meaning -8
- Instead, first **extend** A to five bits
  - **{1'b0,A}** – e.g., 1000 becomes 01000
- Then convert to signed
  - \$signed({1'b0,A}) – e.g., 01000 as 5-bit signed number is still 8 (due to 0 in highest-order bit)
- Operands of "<" automatically sign-extended to widest operand's width
  - So B extended to 5-bits with sign bit preserved
- Comparison is thus correct

```
module Testbench();
```

```
    reg [3:0] A_s;
```

```
    reg signed [3:0] B_s;
```

```
    wire Gt_s, Eq_s, Lt_s;
```

```
    Comp4 CompToTest(A_s, B_s, Gt_s, Eq_s, Lt_s);
```

```
    initial begin
```

```
        A_s = 4'b0011; B_s = 4'b0001;
```

```
        #10 A_s = 4'b1111; B_s = 4'b0111;
```

```
        #10 A_s = 4'b0111; B_s = 4'b1011;
```

```
        #10 A_s = 4'b0001; B_s = 4'b0010;
```

```
        #10 A_s = 4'b0001; B_s = 4'b0001;
```

```
        #10 A_s = 4'b0000; B_s = 4'b1111;
```

```
        #10 A_s = 4'd1; B_s = -4'd1;
```

```
        #10 A_s = 4'd1; B_s = -4'd8;
```

```
    endmodule
```

- Testbench should test multiple values for inputs A and B
  - Should perform comparisons for both positive and negative values of B
  - Should have at least one test case in which A is greater than, less than, and equal to B
- Note that reg variable B\_s, used to connect with B, defined as **signed**
- Vectors illustrate use of binary constants as well as decimal constants
  - Negative binary constant achieved using 1 in high-order bit (two-'s complement form)
  - Negative decimal constant requires negative sign "-" in front of constant

- Simulation

- First two vectors compare positive values for both inputs

- $0011 > 0001 \rightarrow Gt\_s = 1$
- $1111 > 0111 \rightarrow Gt\_s = 1$

- Third test compares A with negative B

- $0111 > 1011 \rightarrow Gt\_s = 1$   
–  $7 > -5$

- Fourth and fifth test should result in the Lt\_s and Eq\_s output asserted, respectively

- $0001 < 0010 \rightarrow Lt\_s = 1$
- $0001 = 0001 \rightarrow Eq\_s = 1$

- Next test compares 0 to -1

- $0000 > 1111 \rightarrow Gt\_s = 1$

- Next test compare 1 to -1

- Last test compares 1 to -8

```
A_s = 4'b0011; B_s = 4'b0001;
#10 A_s = 4'b1111; B_s = 4'b0111;
#10 A_s = 4'b0111; B_s = 4'b1011;
#10 A_s = 4'b0001; B_s = 4'b0010;
#10 A_s = 4'b0001; B_s = 4'b0001;
#10 A_s = 4'b0000; B_s = 4'b1111;
#10 A_s = 4'd1; B_s = -4'd1;
#10 A_s = 4'd1; B_s = -4'd8;
```

- Unintentional use of one of many of Verilog's automatic conversions
  - `B_s <= -4'd15`
  - `-4d'15`
    - 4-bit decimal 15 would be 1111
    - Negative of 1111 (15) is 10001 (-15) – Automatically converted to 5 bits
    - Assignment to B\_s drops the high-order bit, making B\_s=0001
  - Many similar types of automatic conversions in Verilog
  - Use great caution

# Decoders

3-to-8 decoder  
*assign*

```
module decode3to8 (output [7:0] y, input [2:0]a);  
assign y[0] = ~a[2] & ~a[1] & ~a[0];  
assign y[1] = ~a[2] & ~a[1] & a[0];  
assign y[2] = ~a[2] & a[1] & ~a[0];  
assign y[3] = ~a[2] & a[1] & a[0];  
assign y[4] = a[2] & ~a[1] & ~a[0];  
assign y[5] = a[2] & ~a[1] & a[0];  
assign y[6] = a[2] & a[1] & ~a[0];  
assign y[7] = a[2] & a[1] & a[0];  
endmodule
```

3-to-8 decoder  
*for loop*

```
module decode3to8 (output reg [7:0] y, input [2:0]a);  
integer i;  
always @ (*)  
    for (i = 0; i <= 7; i = i + 1)  
        if (a == i)  
            y[i] = 1;  
        else  
            y[i] = 0;  
endmodule
```