

# QUESTION ①

11

(a) Consider the first section of the transposed line:

The flux linking conductor 'a',  $\lambda_a$  is given by the sum of the fluxes produced by 'a', 'b' and 'c': -

$$\lambda_{a1} = \frac{\mu_0}{2\pi} I_a \ln\left(\frac{D_p}{r'}\right) + \frac{\mu_0}{2\pi} I_b \ln\left(\frac{D_p}{D}\right) + \frac{\mu_0}{2\pi} I_c \ln\left(\frac{D_p}{2D}\right)$$

In the middle section:

$$\lambda_{a2} = \frac{\mu_0}{2\pi} I_a \ln\left(\frac{D_p}{r'}\right) + \frac{\mu_0}{2\pi} I_b \ln\left(\frac{D_p}{D}\right) + \frac{\mu_0}{2\pi} I_c \ln\left(\frac{D_p}{D}\right)$$

and in the third section:

$$\lambda_{a3} = \frac{\mu_0}{2\pi} I_a \ln\left(\frac{D_p}{r'}\right) + \frac{\mu_0}{2\pi} I_b \ln\left(\frac{D_p}{2D}\right) + \frac{\mu_0}{2\pi} I_c \ln\left(\frac{D_p}{D}\right)$$

Summing the 3 components and averaging: -

$$\lambda_a = \frac{\mu_0}{2\pi} \cdot \frac{1}{3} \left[ 3 I_a \ln\left(\frac{D_p}{r'}\right) + 2(I_b + I_c) \ln\left(\frac{D_p}{D}\right) + (I_b + I_c) \ln\left(\frac{D_p}{2D}\right) \right]$$

for balanced systems  $I_a = -I_b - I_c$

$$\lambda_a = \frac{\mu_0 I_a}{6\pi} \left[ 3 \ln\left(\frac{D_p}{r'}\right) - 2 \ln\left(\frac{D_p}{D}\right) - \ln\left(\frac{D_p}{2D}\right) \right]$$

$$= \frac{\mu_0 I_a}{6\pi} \left[ \ln\left(\frac{D_p^3}{r'^3}\right) + \ln\left(\frac{D^2}{D_p}\right) + \ln\left(\frac{2D}{D_p}\right) \right]$$

$$= \frac{\mu_0 I_a}{6\pi} \left[ \ln\left(\frac{D_p^3}{r'^3} \times \frac{D^2}{D_p} \times \frac{2D}{D_p}\right) \right] = \frac{\mu_0 I_a}{6\pi} \ln\left(\frac{2D^3}{r'^3}\right)$$

$$= \frac{\mu_0 I_a}{2\pi} \left[ \frac{1}{3} \ln\left(\frac{2D^3}{r'^3}\right) \right] = \frac{\mu_0 I_a}{2\pi} \ln\left(\frac{3\sqrt{2} D}{r'}\right)$$

## QUESTION ① (CONTINUED)

2

$$\text{Now } L_a = \frac{\lambda_a}{I_a} = \frac{\mu_0}{2\pi} \ln \frac{\sqrt[3]{2} D}{r'} \quad \textcircled{6}$$

(b) (i) For a line having a single solid conductor per phase with a radius of 12mm:-

$$\text{GMR} = 0.7788 \times 12 = 9.35 \text{ mm} \equiv 0.00935 \text{ m}$$

The geometric mean distance between phases is:

$$\text{GMD} = \sqrt[3]{2} \cdot 1.5 = 1.89 \text{ m}$$

Hence the inductance per phase per metre is:-

$$\frac{\mu_0}{2\pi} \ln \left( \frac{\text{GMD}}{\text{GMR}} \right) = \frac{\mu_0}{2\pi} \ln \left( \frac{1.89}{0.00935} \right) = 1.062 \times 10^{-6} \text{ H/m}$$

For a 20km line:

$$L_{\text{TOT}} = 1.062 \times 10^{-6} \times 20000 = \underline{\underline{0.0212 \text{ H}}} \quad \textcircled{4}$$

(ii) For a line having stranded conductors:

$$\text{GMR} = 16 \sqrt{(r' \cdot d \cdot d \cdot \sqrt{2} d)^4} = \sqrt[4]{r' d^3 \sqrt{2}} = 10.3 \text{ mm} \equiv 0.0103 \text{ m}$$

GMR remains unchanged from (i)

$$\therefore L = \frac{\mu_0}{2\pi} \ln \left( \frac{1.89}{0.0103} \right) = 1.042 \times 10^{-6} \text{ H/m}$$

$\therefore$  For the 20km line:

$$L_{\text{TOT}} = 1.042 \times 10^{-6} \times 20000 = \underline{\underline{0.0208 \text{ H}}} \quad \textcircled{4}$$


(c) For a 20km long line operating at 50Hz:

$$\text{Resistance} = 20 \times 0.04 = 0.8 \Omega$$

$$\text{Reactance} = 2\pi \times 50 \times 0.0208 = 6.53 \Omega$$

# QUESTION ① (CONTINUED)

3

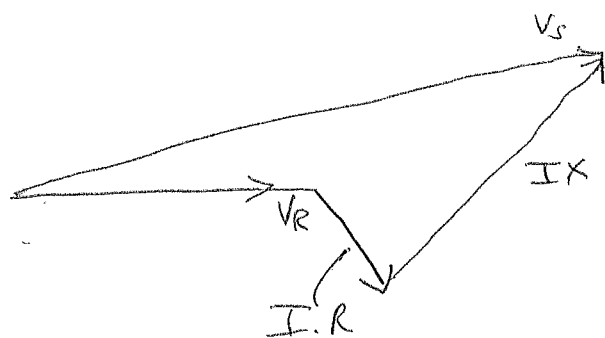

$$V_s^2 = (V_R + I.R \cos \phi + I.X \sin \phi)^2 + (I.X \cos \phi - I.R \sin \phi)^2$$

$$\text{Now } V_R = \frac{33000}{\sqrt{3}} = 19052.6 \text{ V}$$

$$\text{and since } P = \sqrt{3} V_L I_L \cos \phi$$

$$\text{then } I_L = \frac{900 \times 10^3}{\sqrt{3} \cdot 33000 \cdot 0.9} = 17.5 \text{ A}$$

$$\begin{aligned} \therefore V_s^2 &= [19052.6 + (17.5 \times 0.8 \times 0.9) + (17.5 \times 6.53 \times 0.436)]^2 \\ &\quad + [(17.5 \times 6.53 \times 0.9) - (17.5 \times 0.8 \times 0.436)]^2 \\ &= [19052.6 + 12.6 + 49.82]^2 + [102.85 - 6.104]^2 = 19115^2 + 96.75^2 \end{aligned} \quad (4)$$

$$\therefore V_s = 19115 \text{ V (phase)} \quad \underline{\underline{V_{SL} = 33108 \text{ (line)}}}$$


(d) The reason for using bundled conductors on HV lines is to further increase the GMR and therefore reduce the reactance of the line. It also reduces the likelihood of corona discharge by reducing the electric field gradient. (2)

## QUESTION 2

4

(a)(i) Protection is needed to save personnel from risk of electrocution and to help prevent risk of fire or explosion and damage to plant. ①

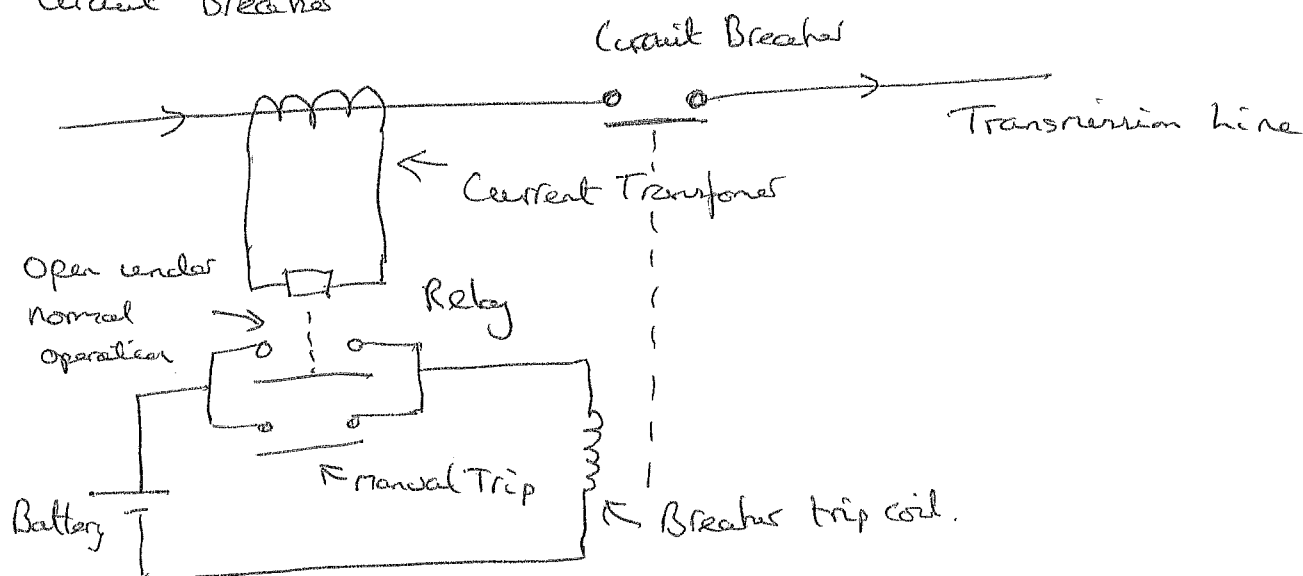(ii) Protection systems are made up of 3 key components:  
Instrument transformer  
Relay  
Circuit Breaker



When overcurrent detected relay closes trip contacts (or these can be closed manually) causing current to flow through trip coil, opening the CB contacts. ③

(b) Buchholz Relay


In oil immersed transformers an internal fault is always accompanied by the release of gas, since oil temperature is increased to vapourising point in the vicinity of the fault. Since some faults (eg. earth fault close to the neutral point involving only a few turns) produce insufficient fault current to operate the protection relays, a gas operated relay is used.

This consists of 2 pivoted buckets carrying mercury tilt switches. When a slight fault occurs gas is trapped in the relay housing. As the gas accumulates
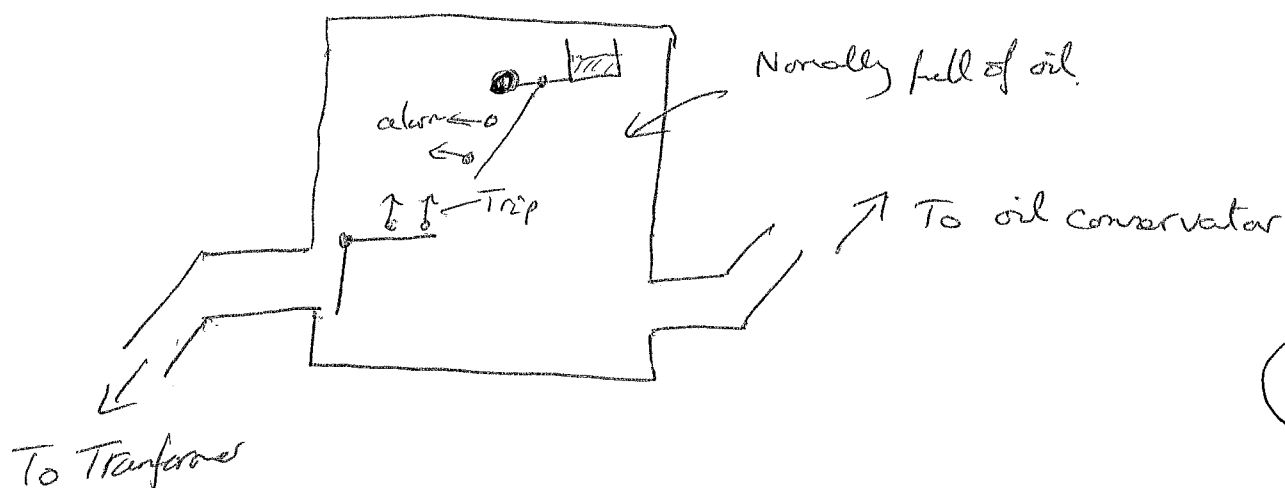
## QUESTION 2 (CONTINUED)

5

the oil level in the relay falls. This causes the bucket to tilt and completes the alarm circuit. When a serious fault occurs a sudden surge of gas ripples on the lower bucket causing it to tilt the mercury switch, closing the circuit to trip the circuit breaker.



- (c) Tap changing transformers are used to compensate for varying voltage drops in the system caused by load fluctuations, and also to control reactive power flow over transmission lines. A transformer which can alter its voltage ratio, either automatically or manually whilst carrying the load current is called an on-load tap changing transformer. An off-load tap changing transformer needs to be disconnected and isolated (ie off-load) before the taps can be changed, which can cause a disruption to the supply.

- (d) For the 2 circuits to be electrically equivalent the no-load transformation ratios and the short circuit impedances must be equal.

1. no-load voltages:

Primary to Secondary

$$K = \frac{A}{A+C}$$

(1)

## QUESTION 2 (CONTINUED)

6

Secondary to Primary:

$$\frac{1}{R} = \frac{B}{B+C} \quad (2)$$

Short circuit impedances:

Impedance measured at primary with secondary short circuited:

$$Z = \frac{AC}{A+C} \quad (3)$$

Impedance measured at secondary with primary short circuited

$$\frac{Z}{R^2} = \frac{BC}{B+C} \quad (4)$$

From (1) and (3):  $C = Z/k$

Back substituting in (1):  $R = \frac{A}{A + \frac{Z}{R}} = \frac{RA}{RA + Z}$

$$\therefore A = \frac{Z}{1-R}$$

Back substituting in (2):

$$\frac{1}{R} = \frac{B}{B + \frac{Z}{R}} \Rightarrow B = \frac{Z}{R(R-1)} \quad (4)$$

(e) On the nominal tap  $Z_{HL} = j0.08 p.u$   $k=1$

On the  $\pm 10\%$  tap  $Z'_{HL} = k^2 \cdot Z_{HL} = 1.1^2 \cdot 0.08 = j0.0968$



$$\therefore A = \frac{Z}{1-R} = \frac{j0.0968}{-0.1} = -j0.968$$

$$B = \frac{Z}{R(R-1)} = \frac{j0.0968}{1.1 \times 0.1} = j0.88$$

$$C = \frac{Z}{R} = \frac{j0.0968}{1.1} = j0.088$$

# QUESTION 2 (CONTINUED)

7

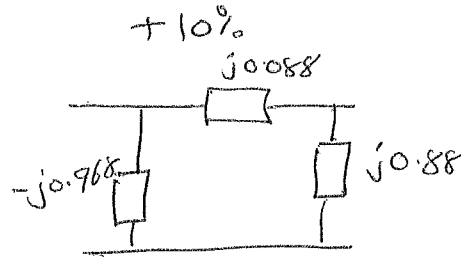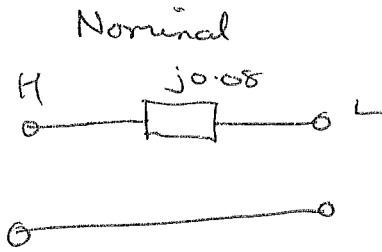


4

(f) Converting Grid Infeed to 100 MVA base:

$$Z_{sys} = \frac{100}{1000} \times j1.0 = j0.1 \text{ pu}$$

Nominal tap:

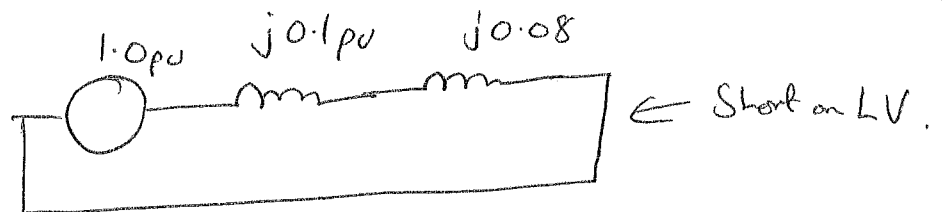


$$I_{f \text{ pu}} = \frac{1.0}{j0.18} = -j5.56$$

$$I_{\text{base at fault}} = \frac{100 \times 10^6}{\sqrt{3} \times 66 \text{ kV}} = 875 \text{ A} \quad 437 \text{ A}$$

$$\therefore |I_f| = \frac{4868 \text{ A}}{2} = 2429.7$$

For the +10% tap:

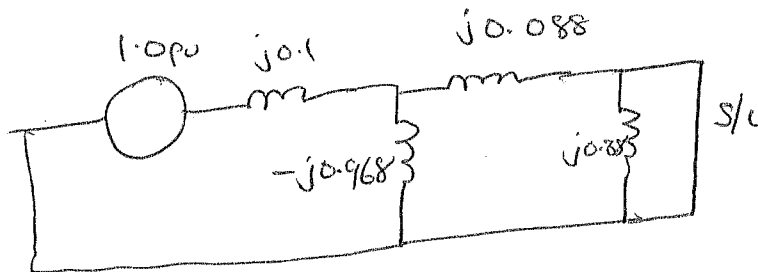

$$I_f = \frac{1.0}{j(0.1 + 0.0968)} = -j5.08 \text{ pu}$$

$$\therefore |I_f| = I_{\text{base}} \times I_{f \text{ pu}} = \frac{4475 \text{ A}}{2}$$


$$2220 \text{ A}$$

3

### QUESTION 3

8

(a)

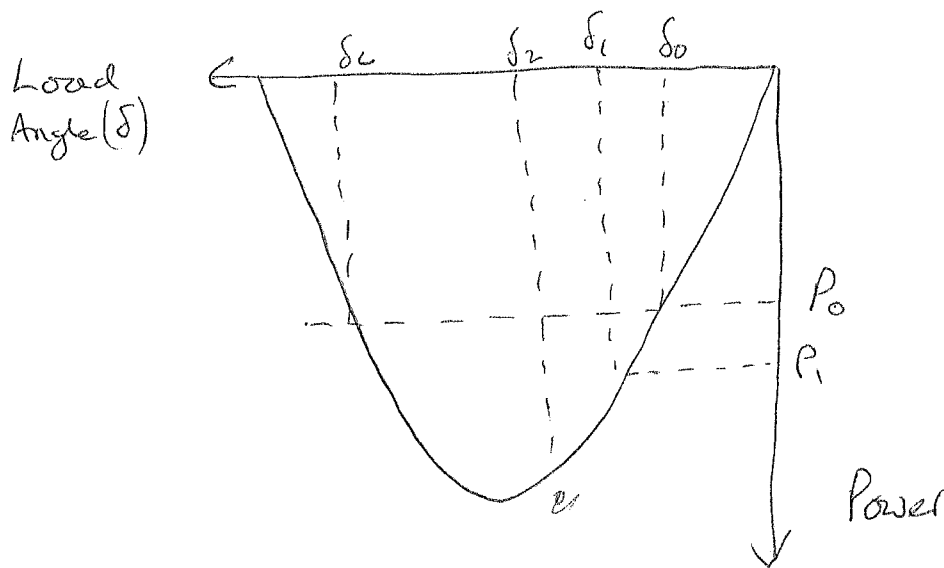


Assume initially the motor is delivering mechanical power  $P_0$  at a load angle  $\delta_0$ . The load suddenly increases to  $P_1$ . Due to machine inertia  $\delta_0$  does not alter instantaneously to the value required to transmit the required electrical power to the motor. Therefore the rotor slows down and the speed falls below the synchronous speed and  $\delta$  increases. As  $\delta$  increases towards  $\delta_1$ , the power difference decreases. The power difference at  $\delta_1$  is zero and hence the acceleration is zero. However the velocity relative to the synchronous speed is not zero and  $\delta$  will continue to increase. However now the electrical power is greater than the mechanical load so the rotor accelerates with a steady reduction in the rate of increase of  $\delta$ . When the rotor attains synchronous speed  $\delta$  stops increasing (max overshoot of  $\delta$  is  $\delta_2$ ). Since  $P_e > P_m$  the rotor speed increases above synchronous speed and  $\delta$  falls below  $\delta_2$ . With no damping  $\delta$  oscillates between  $\delta_0$  and  $\delta_2$ . If  $\delta_2$  exceeds  $\delta_c$  then stability will be lost.



### QUESTION 3 (CONTINUED)

9

(b)

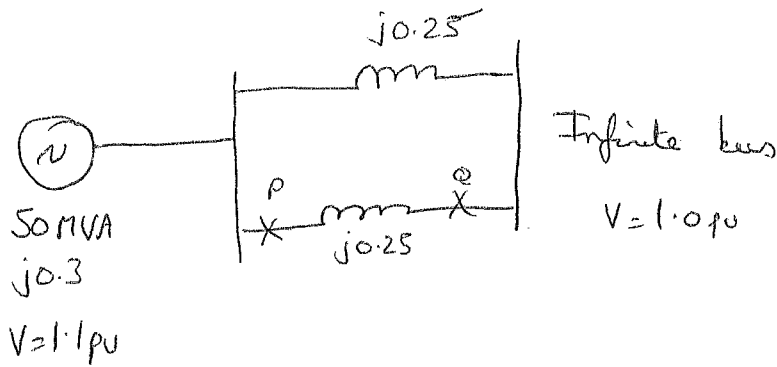

(i) Before the fault the total system reactance is:

$$j0.3 \parallel j0.25 = j0.425 \text{ pu}$$

Now since  $P_{eb} = \frac{V_s V_r}{X} \sin \delta$

$$P_{eb} = \frac{1.1 \times 1.0}{0.425} \sin \delta = \underline{\underline{2.59 \sin \delta}}$$

Expressing the load as a pu value:

$$\frac{40 \text{ MW}}{50 \text{ MVA}} = 0.8 \text{ pu.}$$

Therefore the pre-fault load angle may be found:

$$0.8 = 2.59 \sin \delta \Rightarrow \delta = \underline{\underline{18.0^\circ (0.314 \text{ rad})}} \quad (3)$$

(ii) During the fault the new power-load angle equation becomes:

$$P_{ed} = \frac{1.1 \times 1.0 \sin \delta}{1.2} = \underline{\underline{0.917 \sin \delta}} \quad (1)$$

(iii) After the fault has been cleared the system reactance is:


$$j0.3 + j0.25 = j0.55 \text{ pu}$$

# QUESTION 3 (CONTINUED)

10

$$P_{ea} = \frac{1.1 \times 1.0 \sin \delta}{0.55} = \underline{\underline{2 \sin \delta}}$$

①

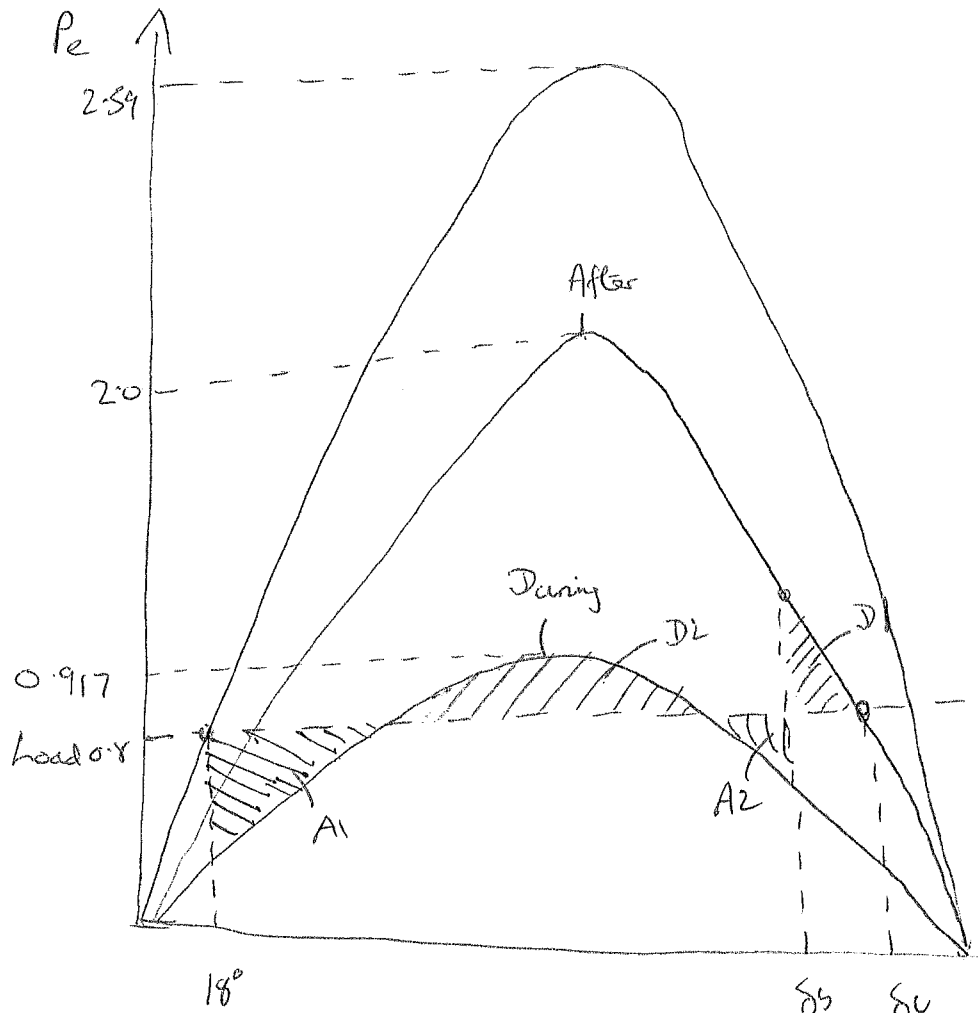

④

A1 + A2 Accelerating areas

D1 + D2 Decelerating areas

$\delta_s$   $\delta_c$   
 $\uparrow$   $\downarrow$  Critical angle  
 Critical decrease  
 angle

For the equal area criteria:

$$\text{Accelerating Area} = \text{Decelerating Area}$$

$$\delta_c = \arcsin\left(\frac{0.8}{2}\right) = 180^\circ - 23.6^\circ = 156.4^\circ \quad (2.729 \text{ rad})$$

$$\int_{\delta_s}^{\delta_c} (P_m - 0.917 \sin \delta) d\delta = \int_{\delta_s}^{\delta_c} (2.0 \sin \delta - P_m) d\delta$$

### QUESTION 3 (CONTINUED)

11

$$\therefore \begin{bmatrix} 0.85 + 0.917 \cos \delta \\ -\delta_0 \end{bmatrix}_{\delta_s}^{\delta_s} = \begin{bmatrix} -2 \cos \delta - 0.85 \\ -\delta_s \end{bmatrix}_{\delta_s}^{\delta_c}$$

$$\begin{aligned} \therefore \cancel{0.85} \delta_s + 0.917 \cos \delta_s - 0.85 \delta_0 - 0.917 \cos \delta_0 \\ = -2 \cos \delta_c - 0.85 \delta_c + 2 \cos \delta_s + \cancel{0.85} \delta_s \end{aligned}$$

$$\therefore 1.083 \cos \delta_s = 0.8 (\delta_c - \delta_0) - 0.917 \cos \delta_0 + 2 \cos \delta_c$$

$$\begin{aligned} 1.083 \cos \delta_s &= 0.8 (2.729 - 0.314) - 0.872 - 1.833 \\ &= 0.773 \end{aligned}$$

$$\therefore \underline{\underline{\delta_s = 135^\circ}}$$

5

(d) The transient stability could be enhanced by:

- (i) Increasing the system voltage
- (ii) Reducing the system reactance
- (iii) Using faster circuit breakers
- (iv) Increasing the generator inertia constant

2

Generator A: - All values already given on base of 30MVA

Generator G:

$$X_+ = j0.1 \times \frac{30}{50} \times \frac{22^2}{25^2} = j0.0465 \text{ pu}$$

$$X_- = j0.08 \times \frac{30}{50} \times \frac{22^2}{25^2} = j0.0372 \text{ pu}$$

$$X_0 = j0.05 \times \frac{30}{50} \times \frac{22^2}{25^2} = j0.0232 \text{ pu}$$

Transformer B: Already on correct base

Transformer C:

$$X_+ = X_- = X_0 = j0.3 \times \frac{30}{40} = j0.225 \text{ pu}$$

Lines D and E:

$$Z_{\text{base}} = \frac{(132000)^2}{30 \times 10^6} = 581 \Omega$$

$$\therefore X_+ = X_- = \frac{j20}{581} = j0.0344 \text{ pu}$$

$$X_0 = \frac{j30}{581} = j0.0516 \text{ pu}$$




Transformer F: Already on correct base.

4

# QUESTION 4 (CONTINUED)

13



(b) Positive Sequence diagram

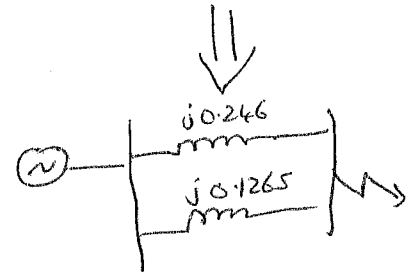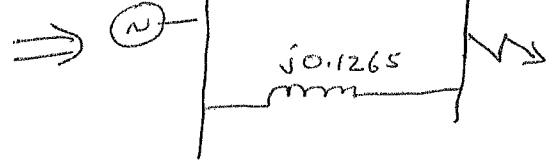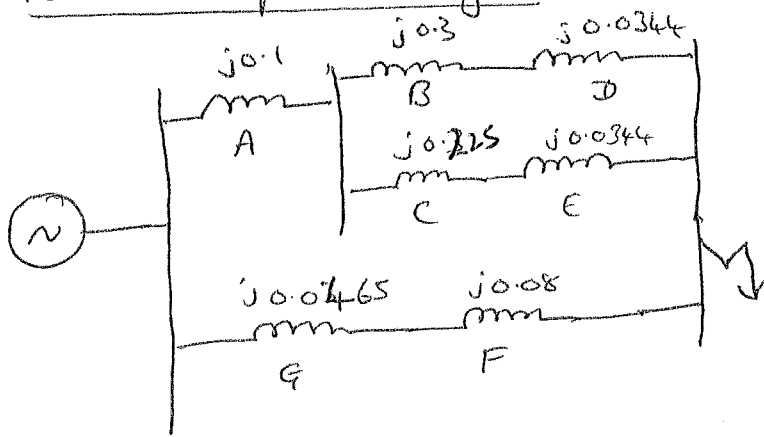

$$Z_+ = j0.0836 \text{ pu}$$




Negative Sequence diagram.

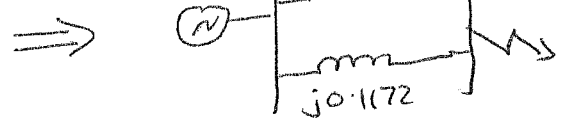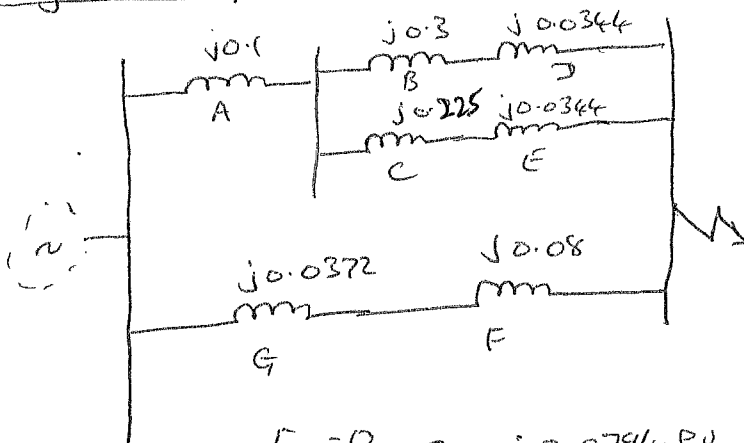

$$E_- = 0 \quad Z_- = j0.0794 \text{ pu}$$




Zero Sequence diagram

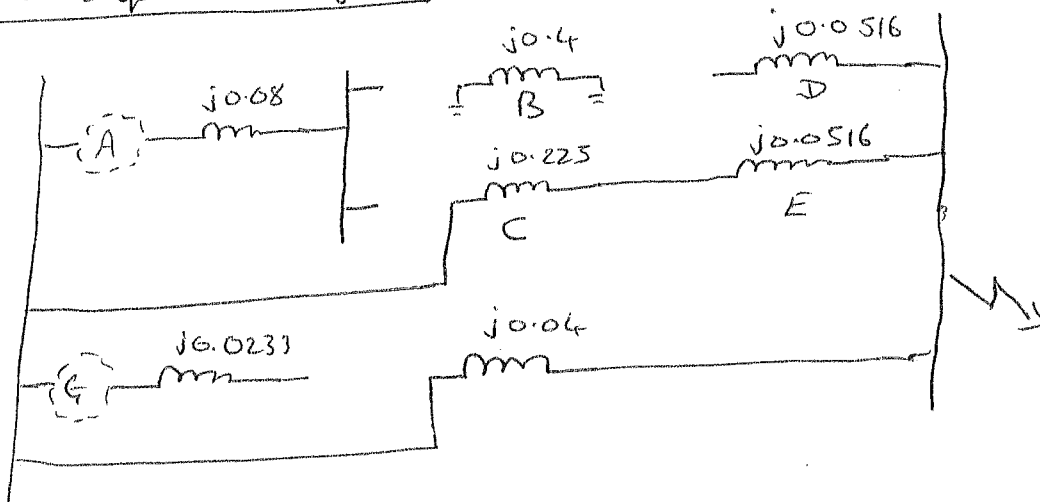


7

# QUESTION 4 (CONTINUED)

14

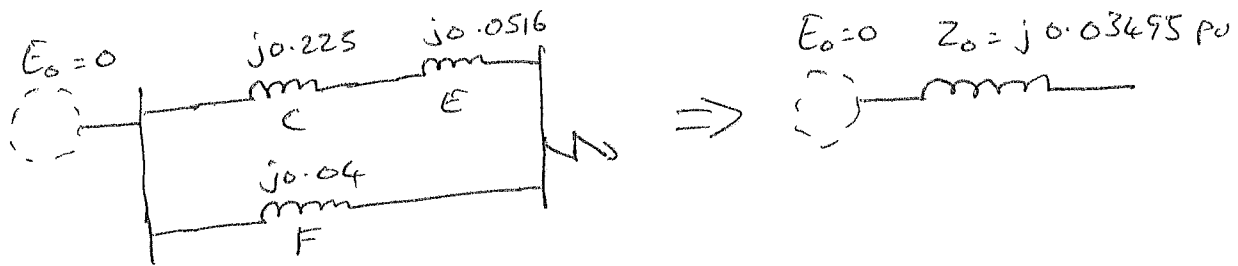

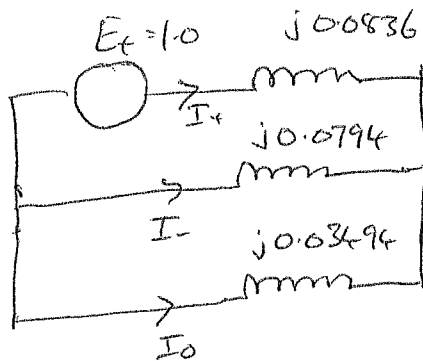- (c) For a 2 phase to Earth fault connect the sequence networks in parallel:



$$I_+ = \frac{1.0}{j0.0836 + (j0.0794 \parallel j0.03494)} = \frac{1}{j0.1078} = -j9.28 \text{ pu}$$

$$I_- = -I_+ \cdot \frac{j0.03494}{(j0.03494 + j0.0794)} = -(-j9.28) \times 0.306 = j2.84 \text{ pu}$$

$$I_0 = -I_+ - I_- = j6.44 \text{ pu}$$

$$I_A = I_0 + I_+ + I_- = -j9.28 + j2.84 + j6.44 = 0 \text{ (As expected)}$$

$$I_B = I_0 + a^2 I_+ + a I_- = j6.44 + 1 \angle 240^\circ (-j9.28) + 1 \angle 120^\circ (j2.84) = -10.5 + j9.66 \text{ pu}$$

$$I_C = I_0 + a I_+ + a^2 I_- = j6.44 + 1 \angle 120^\circ (-j9.28) + 1 \angle 240^\circ (j2.84) = 10.5 + j9.66 \text{ pu}$$

$$\therefore \text{Total fault current} = I_B + I_C = -10.5 + 10.5 + j9.66 + j9.66 = j19.32 \text{ pu}$$

Base current at point of fault

$$= \frac{MVA_b}{\sqrt{3}V_b} = \frac{30 \times 10^6}{\sqrt{3} \times 132 \times 10^3} = 131.2 \text{ A}$$

$$\therefore \text{Magnitude of total fault current} = 131.2 \times 19.32 = \underline{\underline{2535 \text{ A}}}$$

Sequence voltages at fault:

$$V_+ = V_- = V_0 = 1.0 - (-j9.28)(j0.0836) = 0.225 \text{ pu}$$

$$V_A = V_0 + V_+ + V_- = 3 \cdot 0.225 = 0.675 \text{ pu}$$

$$\begin{aligned} \text{(check } V_B &= V_0 + a^2 V_+ + a V_- = 0.225 + 1 \angle 240^\circ \cdot 0.225 + 1 \angle 120^\circ \cdot 0.225 = 0 \\ V_C &= V_0 + a V_+ + a^2 V_- = 0.225 + 1 \angle 120^\circ \cdot 0.225 + 1 \angle 240^\circ \cdot 0.225 = 0 \end{aligned}$$

$$\text{Base phase voltage} = \frac{132 \times 10^3}{\sqrt{3}} = 76.2 \text{ kV}$$

$$\therefore V_{Aph} = 0.675 \cdot 76.2 = 51.4 \text{ kV}$$

$$\text{Hence } \underline{\underline{|V_{AB}| = 51.4 \text{ kV} \quad |V_{CA}| = 51.4 \text{ kV}}}$$

8

(d). Since generator A plays no part in the zero sequence diagram the addition of a star point reactor will have no effect on the fault current.

1