

## Solutions

### Q1.a

The Insertion Loss ( $IL$ ) is the ratio of transmitted power  $P_t$  to the incident power  $P_{in}^+$


$$IL = -10 \log \left( \frac{P_t}{P_{in}^+} \right) = -10 \log \left( \frac{P_{in}^+ - P_{in}^-}{P_{in}^+} \right) = -10 \log (1 - |\Gamma_{in}|^2) \quad (1 \text{ mark})$$

The fraction of the incident power that is absorbed by the load, is missing from the signal returned to the generator. This “loss” is called the return loss ( $RL$ )

$$RL = -10 \log \left( \frac{P_{in}^-}{P_{in}^+} \right) = -10 \log |\Gamma_{in}|^2 = -20 \log |\Gamma_{in}| \quad (1 \text{ mark})$$
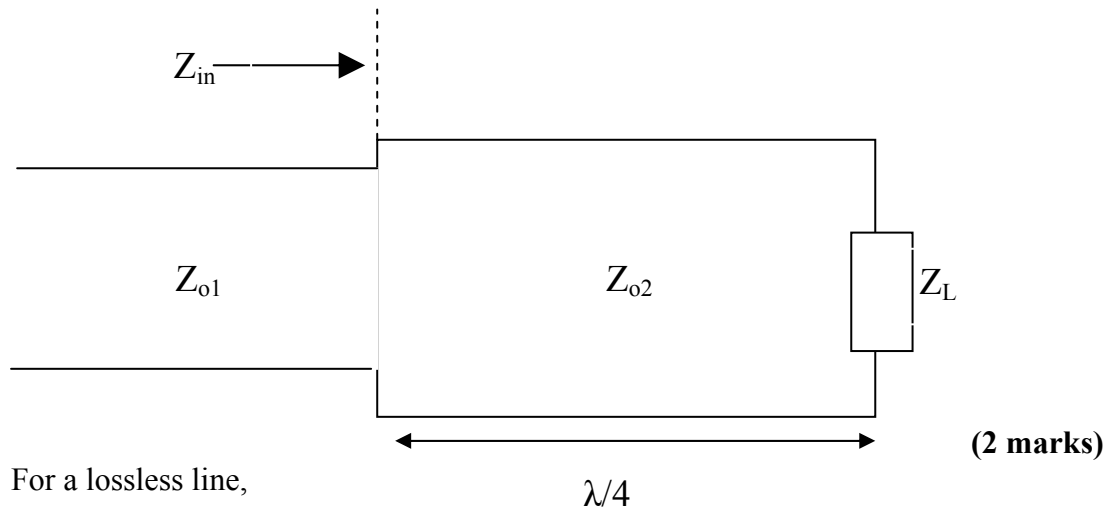
### Q1.b

Usually used as an intermediate matching between two transmission lines of different real characteristic impedances. For matching over a narrow band of frequency  $f$  ( $\pm 5\%$ ), a single section is adequate but 2 or more sections are required for broadband matching. (1 mark)



For a lossless line,

$$Z_{o2} = \sqrt{Z_{o1} Z_L}$$

for real  $Z_{o1}$ ,  $Z_{o2}$  and  $Z_L$ .

(1 mark)

### Q1.c

$$\Gamma_{load} = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{(50 + j80) - 50}{(50 + j80) + 50} = 0.39 - j0.49 \quad (1 \text{ mark})$$

$$\beta = \frac{2\pi}{\lambda} = 0.628 \quad (1 \text{ mark})$$

$$Z_{in} = Z_o \frac{Z_L + jZ_o \tan(\beta l)}{Z_o + jZ_L \tan(\beta l)} = 11.7 - j6.3 \Omega \quad (1 \text{ mark})$$

$$\Gamma_{in} = \frac{Z_{in} - Z_o}{Z_{in} + Z_o} = -0.6 - j0.17 \quad (1 \text{ mark})$$

$$RL = -20 \log |\Gamma_{in}| = -4.1 \text{ dB} \quad (1 \text{ mark})$$

$$IL = -10 \log (1 - |\Gamma_{in}|^2) = -2.1 \text{ dB} \quad (1 \text{ mark})$$

### **Q1.d**

The distance between successive minima is

$$d = \frac{\lambda}{2}$$

i.e.

$$\lambda = 2d = 4.2 \text{ cm} \quad (1 \text{ mark})$$

$$\beta = \frac{2\pi}{\lambda} = 1.5 \quad (1 \text{ mark})$$

The reflection coefficient is given by

$$\Gamma = \rho e^{j\theta} \quad (1 \text{ mark})$$

where

$$\rho = \frac{VSWR - 1}{VSWR + 1} = 0.5 \quad (1 \text{ mark})$$

At the 1<sup>st</sup> voltage minima, we have

$$0.9\beta - \frac{\theta}{2} = \pi$$

i.e.

$$\theta = 2\pi + 1.8\beta = 9.58 \quad (1 \text{ mark})$$

Therefore at 0.9cm from the load

$$\Gamma_{(0.9 \text{ cm})} = 0.5e^{j9.58} \quad (1 \text{ mark})$$

The reflection coefficient at the load can be obtained as

$$\Gamma_L = \Gamma_{(0.9 \text{ cm})} e^{2j\beta \times 0.9} = 0.5e^{j12.28} = 0.48 - j0.14 \quad (1 \text{ mark})$$

The load impedance can be calculated as

$$Z_L = Z_o \frac{1 - \Gamma_L}{1 + \Gamma_L} = 17 + j6.4 \quad (1 \text{ mark})$$

### **Q2.a**

Impedance representation in the smith chart

$$z = r + jx = \frac{1 + \Gamma_{(d)}}{1 - \Gamma_{(d)}} \quad (1 \text{ mark})$$

represented as

$$y = \frac{I}{z} = \frac{1 - \Gamma_{(d)}}{1 + \Gamma_{(d)}} = \frac{1 + \Gamma_{(d)}e^{-j\pi}}{1 - \Gamma_{(d)}e^{-j\pi}} \quad (1 \text{ mark})$$

This shows that the Smith chart can be used to find transformation of admittance as well as impedance. This can be achieved by rotating an arc with a radius of  $\Gamma_{(d)}$  through an angle of  $180^\circ (\equiv 0.25\lambda)$ .

**(2 marks)**

### **Q2.b**


$$z_L = \frac{(150 + j30)}{50} = 3 + j0.6$$

(point A) (1 mark)

i.e.

$$y_L = 0.31 - j0.07$$

(point B) (1 mark)

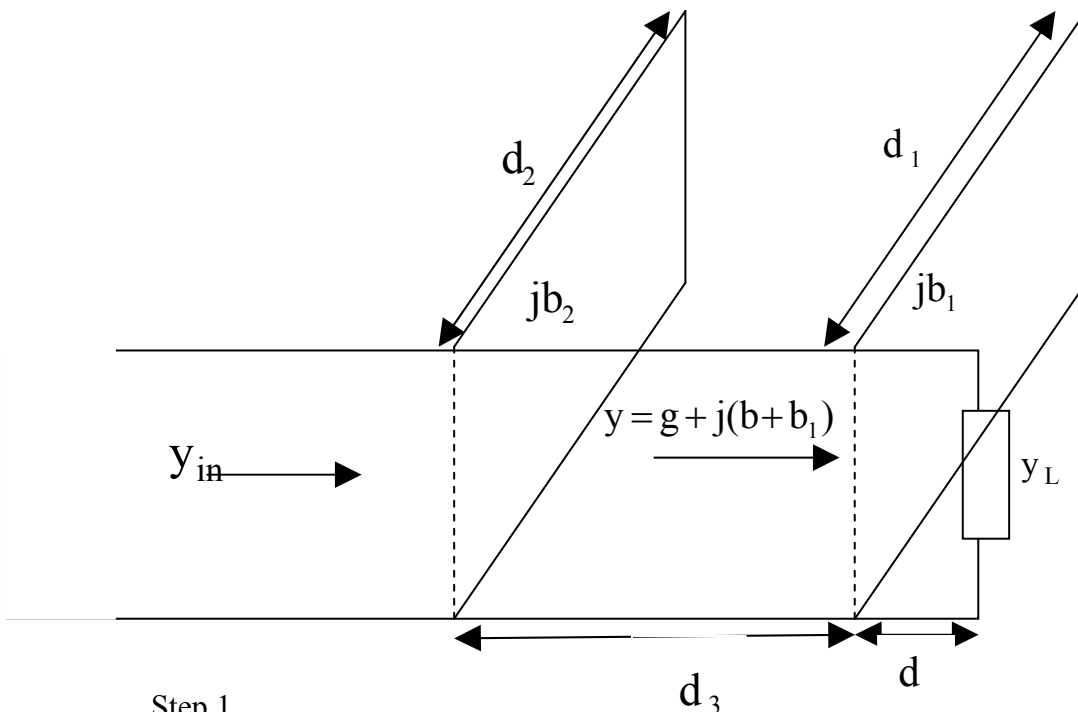

Step 1

Rotate the unit  $g$  circle *Towards Load*, by a distance of  $d_3 = 0.125\lambda$ .

(1 mark)

Step 2

Move from point B to intersect the new, rotated, unit circle at point C. The movement should be on the corresponding conductance circle, since the stub does not alter the real part of the admittance.

(1 mark)

Step 3

The admittance at point C is

$$y_C = 0.31 + j0.27$$

compare it with that at B

$$y_L = 0.31 - j0.07$$

shows that stub 1 has provided  $j0.34$ , i.e.  $b_1 = 0.34$ .

(2 marks)

Step 4

For an o.c. stub, this means  $d_1 = 0.052\lambda$ , i.e. the distance from D to E on the chart.

(1 mark)

Step 5

Move a distance  $d_3 = 0.125\lambda$  along the line from the 1<sup>st</sup> stub position to the 2<sup>nd</sup> stub position (from point C to F).

(1 mark)

Step 6

At point F, the admittance is  $y_F=1+j1.3$ , i.e. stub 2 must provide  $-j1.3$  ( $b_2=-1.3$ ) to reach the matched condition. **(1 mark)**

Step 7

For a s.c. stub, this means  $d_2=(0.354-0.25)\lambda=0.104\lambda$ , i.e. the distance from G to H on the chart. **(1 mark)**

### **Q2.c**

$$z_L = \frac{(150 + j30)}{50} = 3 + j0.6 \quad (\text{point A}) \quad \mathbf{(1 \text{ mark})}$$

Moving a distance of  $0.1\lambda$  towards generator take us to point A' on the Smith chart  
 $z_L=0.9-j1.14$  (point A') **(1 mark)**

i.e.

$$y_L=0.42+j0.55 \quad (\text{point B}) \quad \mathbf{(1 \text{ mark})}$$

Step 1

Rotate the unit g circle *Towards Load*, by a distance of  $d_3=0.125\lambda$ . **(1 mark)**

Step 2

Move from point B to intersect the new, rotated, unit circle at point C. The movement should be on the corresponding conductance circle, since the stub does not alter the real part of the admittance. **(1 mark)**

Step 3

The admittance at point C is

$$y_C=0.42+j1.85$$

compare it with that at B

$$y_L=0.42+j0.55$$

shows that stub 1 has provided  $j1.3$ , i.e.  $b_1=1.3$  **(1 mark)**

Step 4

For an o.c. stub, this means  $d_1=0.146\lambda$ , i.e. the distance from D to E on the chart. **(1 mark)**

Step 5

Move a distance  $d_3=0.125\lambda$  along the line from the 1<sup>st</sup> stub position to the 2<sup>nd</sup> stub position (from point C to F). **(1 mark)**


Step 6

At point F, the admittance is  $y_F=1-j2.8$ , i.e. stub 2 must provide  $j2.8$  ( $b_2=2.8$ ) to reach the matched condition. **(1 mark)**

Step 7

For an o.c. stub, this means  $d_2=0.196\lambda$ , i.e. the distance from D to G on the chart. **(1 mark)**

### Q3.a

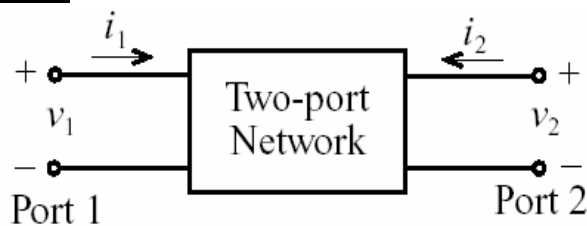

(1 mark)

The transmission matrix, or the ABCD matrix, of a two-port circuit relates the output terminal voltage and current ( $V_2, I_2$ ) to the input voltage and ( $V_1, I_1$ ) current as

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

(1 mark)

In matrix form

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

(1 mark)

( $V_1, I_1$ ) and ( $V_2, I_2$ ) are the actual voltages and currents (*not normalized*), and they are continuous at the boundaries of the two ports. This means the output of one two-port circuit can be considered as the input of another two-port circuit. This makes the ABCD representation useful when cascading two-port networks.

(1 mark)

### Q3.b

Available Power Gain

$$G_A = \frac{P_{avn}}{P_{avs}}$$

(1 mark)

It is the ratio between power available from the network and the power available from the source. In most of the cases this gain is independent of  $Z_L$ . Gain of some active circuits is a function of  $Z_L$ .

(1 mark)

Transducer Power Gain


$$G_T = \frac{P_L}{P_{avs}}$$

(1 mark)

It is the ratio between power available at the load and the power available from the source. This gain depends on both  $Z_g$  and  $Z_L$ .

(1 mark)

### Q3.c

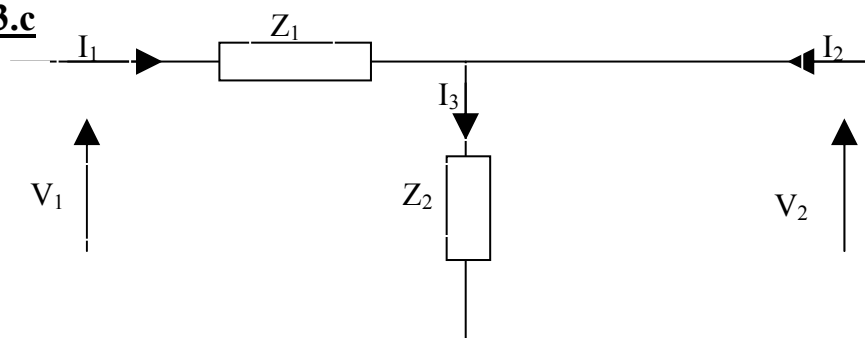

$$V_1 = I_1 Z_1 + I_1 Z_2 + I_2 Z_2 \quad (1 \text{ mark})$$

$$\therefore I_1 = \frac{V_1 - I_2 Z_2}{Z_1 + Z_2} \quad (1 \text{ mark})$$

$$V_2 = I_2 Z_2 + I_1 Z_2 \quad (1 \text{ mark})$$

i.e.

$$V_2(Z_1 + Z_2) = I_2 Z_1 Z_2 + V_1 Z_2$$

Hence

$$V_1 = V_2 \left(1 + \frac{Z_1}{Z_2}\right) - I_2 Z_1 \quad (1 \text{ mark})$$

$$I_1 = \frac{V_2}{Z_2} - I_2 \quad (1 \text{ mark})$$

In matrix form

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 + \frac{Z_1}{Z_2} & Z_1 \\ \frac{1}{Z_2} & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

i.e.

$$A = 1 + \frac{Z_1}{Z_2}, B = Z_1, C = \frac{1}{Z_2}, D = 1 \quad (1 \text{ mark})$$

### **Q3.d**

Assume  $Z_1 = 82.2\Omega$  and  $Z_2 = 14\Omega$ . To calculate  $S_{11}$ , the impedance  $Z_{in1}$  is required when the network is terminated with  $Z_o$ ,

$$Z_{in1} = \left[ \frac{Z_2 \left( Z_1 + \frac{Z_2 Z_o}{Z_2 + Z_o} \right)}{Z_1 + Z_2 + \frac{Z_2 Z_o}{Z_2 + Z_o}} \right]$$

$$Z_{in1} = Z_2 \frac{Z_1 Z_o + Z_1 Z_2 + Z_2 Z_o}{Z_2 Z_o + (Z_2 + Z_o)(Z_2 + Z_1)} = 12.17\Omega \quad (1 \text{ mark})$$

$$S_{11} = \Gamma_{in} = \frac{Z_{in1} - Z_o}{Z_{in1} + Z_o} = 0.6 \quad (1 \text{ mark})$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0}$$

For the 1<sup>st</sup> port

$$V_1 = \sqrt{Z_o} (a_1 + b_1)$$

$$V_2 = \sqrt{Z_o} b_2$$

Therefore

$$\frac{V_1}{V_2} = \frac{(a_1 + b_1)}{b_2} = \frac{(1 + \frac{b_1}{a_1})}{\frac{b_2}{a_1}} = \frac{1 + S_{11}}{S_{21}} \quad (1 \text{ mark})$$

i.e.

$$S_{21} = \frac{V_2}{V_1} (1 + S_{11})$$

$$V_2 = V_1 \frac{Z_p}{(Z_p + Z_1)} \quad (1 \text{ mark})$$

where

$$Z_p = \frac{Z_o Z_2}{(Z_o + Z_2)}$$

Hence

$$\frac{V_2}{V_1} = \frac{Z_o Z_2}{(Z_o Z_2 + Z_1 Z_2 + Z_o Z_1)} \quad (1 \text{ mark})$$

Therefore

$$S_{21} = \frac{2Z_o Z_2^2}{2Z_1 Z_o Z_2 + 2Z_o Z_2^2 + 2Z_2 Z_o^2 + Z_1 Z_2^2 + Z_1 Z_o^2} = 0.046 \quad (1 \text{ mark})$$

Similarly it can be shown that  $S_{12}=0.046$  and  $S_{22}=0.6$

#### **Q4.a**

(i) *Conditional Stability*; the network is potentially unstable and may oscillate for certain combinations of load and source impedance values. (1 mark)

(ii) *Unconditional Stability*; the network is unconditionally stable for any combinations of source and load impedance values. (1 mark)

#### **Q4.b**

Generally transistors presents a significant impedance mismatch, so matching will be achieved over a narrow frequency bandwidth. When bandwidth is an issue, then we design for a gain less than the maximum, imperfect matching, to improve bandwidth.

(1 mark)

Sometimes it is required to design an amplifier with a specific gain, other than the maximum. *Constant gain circles* will be used to facilitate gain design.

(1 mark)

#### **Q4.c**

The power gains can be calculated as follows:

First, find the source and load reflection coefficients

$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = 0.333 \quad (0.5 \text{ mark})$$

$$\Gamma_s = \frac{Z_s - Z_o}{Z_s + Z_o} = 0.2 \quad (0.5 \text{ mark})$$

Next the input and output reflection coefficients are computed via

$$\Gamma_{in} = S_{11} + \frac{S_{21}S_{12}\Gamma_L}{1 - S_{22}\Gamma_L} = 0.33 - j0.62 \quad (1 \text{ mark})$$

$$\Gamma_{out} = S_{22} + \frac{S_{21}S_{12}\Gamma_S}{1 - S_{11}\Gamma_S} = 0.42 - j0.58 \quad (1 \text{ mark})$$

Which can be used to calculate:

Transducer power gain

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)(1 - |\Gamma_L|^2)}{|1 - S_{22}\Gamma_L|^2 |1 - \Gamma_S\Gamma_{in}|^2} = 6.47 \quad (1 \text{ mark})$$

Available power gain

$$G_A = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)}{|1 - S_{11}\Gamma_S|^2 (1 - |\Gamma_{out}|^2)} = 11.6 \quad (1 \text{ mark})$$

Operating power gain

$$G = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - S_{22}\Gamma_L|^2 (1 - |\Gamma_{in}|^2)} = 15.4 \quad (1 \text{ mark})$$

#### **Q4.d**

Since  $S_{12} = 0.0$ ,  $S_{11} < 1$  and  $S_{22} < 1$ , then the transistor is unconditionally stable.

(1 mark)

The matching sections gain can be calculated as

$$G_{S_{\max}} = \frac{1}{1 - |S_{11}|^2} = 2.29 = 3.6dB \quad (1 \text{ mark})$$

$$G_{L_{\max}} = \frac{1}{1 - |S_{22}|^2} = 1.59 = 1.9dB \quad (1 \text{ mark})$$

Since

$$G_o = |S_{21}|^2 = 6.25 = 8.0dB \quad (1 \text{ mark})$$

The overall gain


$$G_{T_{\max}} = 3.6 + 8 + 1.9 = 13.5dB$$

This means there is a 2.5dB gain higher than the design requirements.

Equations (52), (53) and (54) may be used to get

$G_s=3dB$	$g_s=0.88$	$C_s = 0.706 \angle 120^\circ$	$r_s=0.166$
$G_s=2dB$	$g_s=0.69$	$C_s = 0.627 \angle 120^\circ$	$r_s=0.294$
$G_L=1dB$	$g_L=0.81$	$C_L = 0.52 \angle 70^\circ$	$r_L=0.3$
$G_L=0dB$	$g_L=0.64$	$C_L = 0.44 \angle 70^\circ$	$r_L=0.44$



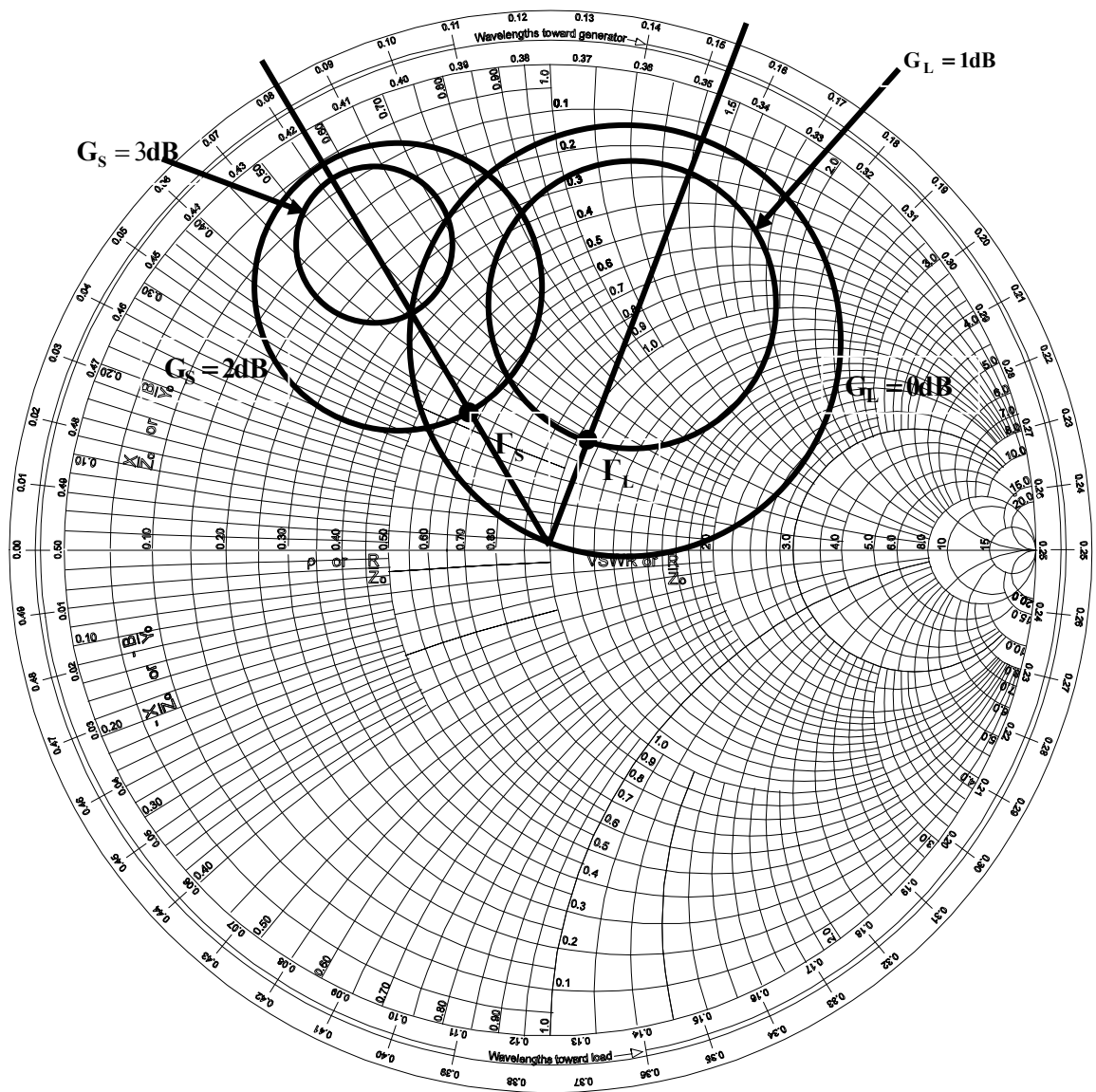

(4 marks,  
1 mark for plotting each circle)

The constant gain circles are plotted on the Smith chart as shown in the figure. For an overall gain of 11dB, we will choose  $G_s = 2\text{dB}$  and  $G_L = 1\text{dB}$ . We select  $\Gamma_s$  and  $\Gamma_L$  along these circles to minimise the distance from the centre of the chart. This will put  $\Gamma_s$  and  $\Gamma_L$  along the radial lines at  $120^\circ$  and  $70^\circ$  respectively. Thus  $\Gamma_s = 0.33 \angle 120^\circ$  and  $\Gamma_L = 0.22 \angle 70^\circ$ .

(2 marks)