

Tutorial Sheet – No 1**(Revision)**

- 1 Perform the following conversions from rectangular to polar form, and vice-versa. (Try these without using any conversion buttons on your calculator to ensure you know the formulas to convert from one coordinate system to the other).

$$\sqrt{3} + j1 = 2\angle 30^\circ$$

$$-3 + j5 = 5.83\angle 121^\circ$$

- 2 Now attempt these examples using your calculator. Ensure you can convert both ways. (Many calculators will perform the conversions at a press of a button, but it is important to know how to do this).

$$3 + j3 = 4.24\angle 45^\circ$$

$$2 + j2\sqrt{3} = 4\angle 60^\circ$$

$$-3 - j4 = 5\angle -126.9^\circ$$

- 3 Hence do the following phasor manipulations and 'discover' the most appropriate method. Give the answers in both polar and rectangular format.

$$3\angle 22^\circ + 4\angle 112^\circ = 5\angle 75.1^\circ = 1.28 + j4.83$$

$$3\angle 22^\circ \times 4\angle 112^\circ = 12\angle 134^\circ = -8.34 + j8.63$$


$$3\angle 22^\circ \div 4\angle 112^\circ = 0.75\angle -90^\circ = 0 - j0.75$$

$$(1 + j2) + (3 + j4) = 4 + j6 = 7.21\angle 56.3^\circ$$


$$(1 + j2) \div (3 + j4) = 0.44 + j0.08 = 0.45\angle 10.3^\circ$$

Hopefully, you will have found that multiplication and division are easier if the phasor is expressed in polar form, and addition and subtraction are easier using j notation. Most calculators make it easy to convert either way, but if your calculator can handle complex numbers directly then presumably conversion is not necessary.

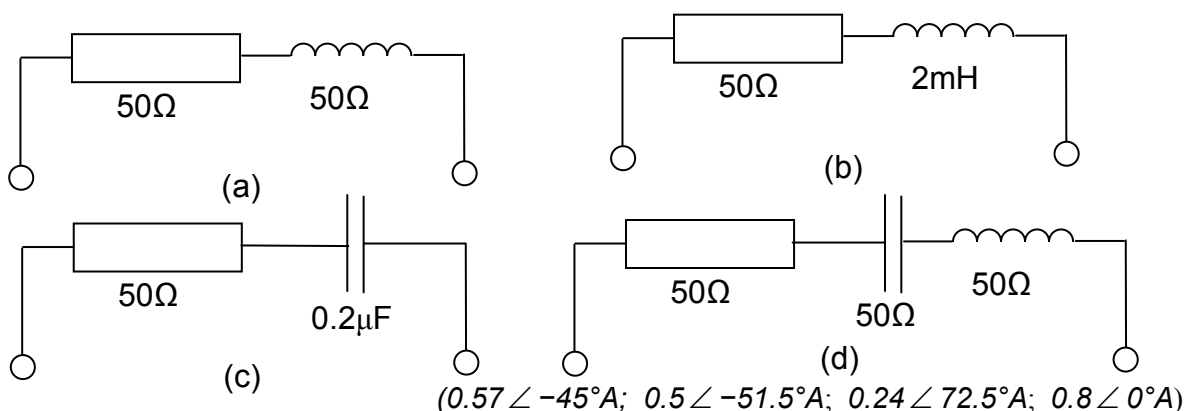
- 4 Calculate the amplitude and phase of the peak current for each of the circuits below, assuming a sinusoidal voltage, having a peak amplitude of 40V and a frequency of 5kHz, is applied.



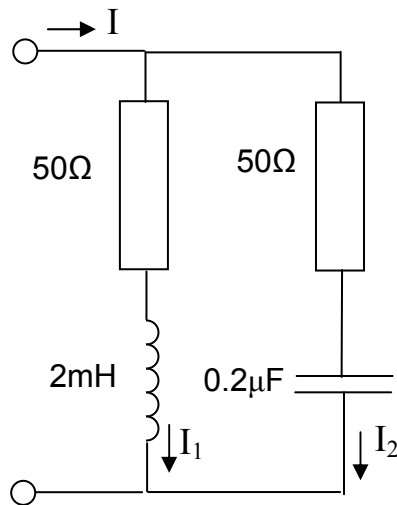- 5 Calculate the amplitude and phase of the input current to each of the following circuits assuming a sinusoidal voltage, having a peak amplitude of 40V and a frequency of 5kHz, is applied.



(a)

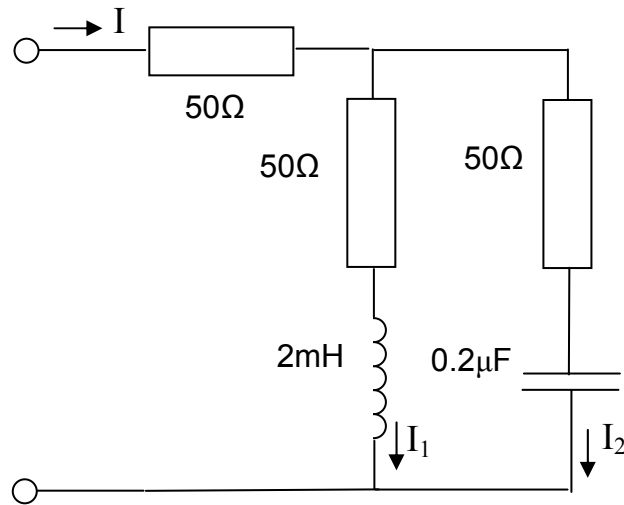

(b)

((a) $0.41 \angle -22^\circ \text{A}$; (b) $0.28 \angle -15.1^\circ \text{A}$)

At the end of this question, if you solved both parts by using the technique where you calculate the input impedance of the branches using $\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2}$ (all impedances in complex form) you will realise that it is a tedious exercise! If in (a) you recognised that the two parallel branches have 40V across them then you could have calculated $\bar{I} = \bar{I}_1 + \bar{I}_2$ where \bar{I}_1 and \bar{I}_2 are calculated as in question 4(b) and 4(c) – a much easier method. In general if you know the voltage across two parallel branches, use the latter method, not the former.