

**Tutorial Sheet – No 4****(Energy and Power)**

**Hint :** In questions 1 and 3, for the quantities to be calculated, initially derive the relevant expressions as general functions of time  $t$  (i.e. only substitute for the given value of  $t$  at the end)

- 1 A circuit consists of a resistance of  $200\Omega$  in parallel with a capacitance of  $1000\mu\text{F}$ . The circuit is supplied by a voltage source  $v(t) = 200t$  Volts, where  $t$  is in seconds from the time of application. At time  $t = 0.5\text{s}$  calculate:
- the instantaneous power dissipated in the resistor
  - the instantaneous power supplied to the capacitor
  - the power supplied by the source
  - the total energy supplied by the source from  $t = 0$  to  $t = 0.5\text{s}$
  - the energy stored in the circuit at  $t = 0.5\text{s}$

(50W; 20W; 70W; 13.3J; 5J)

- 2 A circuit consists of a resistance of  $15\Omega$  in series with an inductance of  $10\text{H}$ . If the circuit is excited by a sinusoidal voltage source of peak value  $100\text{V}$  and frequency  $2\text{Hz}$  calculate the magnitude and phase of the rms current in the circuit, its power factor, and the values of the VA, W and VAR of the circuit.

( $0.56 \angle -83.2^\circ A_{\text{rms}}$ ; 0.118lagging; 39.6VA; 4.67W; 39.3VAR)

- 3 The same circuit from question 2 is now excited by a current source of  $i(t) = 5t$  A, where  $t$  is in seconds from the time the current is applied, calculate the following at  $t = 2\text{s}$ :
- the instantaneous power in the resistance R
  - the instantaneous power input to the inductor
  - the total energy input to the circuit in the time interval  $t = 0$  to  $t = 2\text{s}$
  - the energy stored in the circuit.

(1500W; 500W; 1500J; 500J)

- 4 The total load on an  $11\text{kV}_{\text{rms}}$ ,  $50\text{Hz}$ , single-phase supply consists of:
- an electromagnet, which draws  $9A_{\text{rms}}$  at 0.2 power factor lagging
  - a general load of  $60\text{kVA}$ , operating at 0.6 power factor leading
  - a 90% efficient motor, which is delivering a mechanical output power of  $100\text{kW}$  and is operating at 0.85 power factor lagging

- (a) For each load component calculate the VA, Watts, and VAR demand and input current.

(Electromagnet 99kVA, 19.8kW, 97kVAR,  $9 \angle -78.5^\circ A_{\text{rms}}$ ;  
general load 60kVA, 36kW, -48kVAR,  $5.45 \angle 53.1^\circ A_{\text{rms}}$ ;  
motor 130.7 kVA, 111kW, 68.9kVAR,  $11.88 \angle -31.8^\circ A_{\text{rms}}$ )


- (b) Calculate the resultant VA of the total load and its overall power-factor. Also calculate the total load current and its phase angle.

(Total = 204.3kVA @ 0.82pf lag;  $18.6 \angle -35.2^\circ A_{\text{rms}}$ )

- (c) Calculate the capacitance required to improve the overall load power-factor to 0.95 lagging.

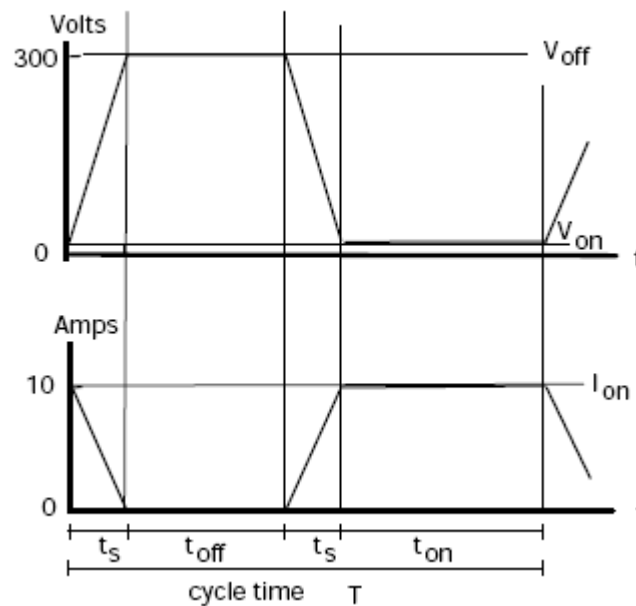(1.66 $\mu\text{F}$ )

- 5 The figure shows one cycle of the voltage across, and the current through, a power-electronic switching device, operating at a frequency of 5kHz. The switch has equal on and off periods  $t_{on}$  and  $t_{off}$  and the two switching events both take a time of  $t_s = 2\mu s$ .



- (a) Neglecting the small ' $V_{on}$ ' volts drop in the switch, derive an expression for the instantaneous  $v_t$  and  $i_t$  during the first switching event of length  $t_s$ .

$$\left( v = V_{off} \frac{t}{t_s}; \quad i = I_{on} \left( 1 - \frac{t}{t_s} \right) \right)$$

- (b) Hence derive an expression for  $p$ , the instantaneous power loss during one switching event, and also its peak value.

$$\left( p = vi = V_{off} I_{on} \left( \frac{t}{t_s} - \frac{t^2}{t_s^2} \right); \quad p_{max} = \frac{1}{4} V_{off} I_{on}; \quad P_{max} = 750W \right)$$

- (c) What temperature rise would the semiconductor have if it had a negligible thermal time-constant and a thermal resistance of  $5^\circ\text{C/W}$  ?

$$(\Delta T = 3750^\circ\text{C} \text{ -not for long !!!})$$

- (d) Show that the average power loss per cycle is given by:

$$P_{av} = \frac{1}{3} \frac{t_s}{T} V_{off} I_{on}$$

- (e) Hence calculate a more realistic temperature rise assuming a thermal time-constant  $\gg 200\text{ms}$

$$(P_{av} = 10W; \Delta T = 50^\circ\text{C})$$

**Note:** In practice thermal time-constants of components are usually  $\gg$  cycle times. Also, whilst the peak instantaneous power loss is independent of the switching time, the average is proportional to  $t_s/T$  – hence it is important to make the switching time as short as possible when designing such circuits.