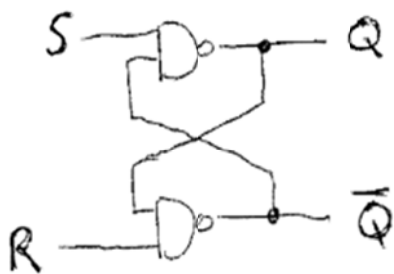


1.



\bar{Q} must be inverse of Q

S	R	Q'
0	0	not allowed
0	1	1
1	0	0
1	1	unchanged

Active low SR latch.


$S=0$ set latch

$R=0$ reset latch

$S=R=1$ no change


$S=R=0$ not allowed as $Q=\bar{Q}=1$

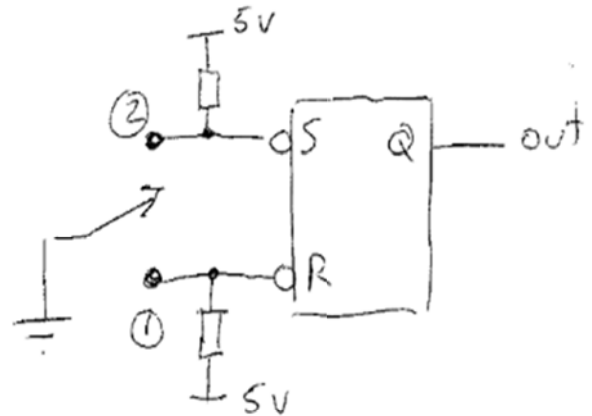SR latch can be used to eliminate 'contact bounce' in a switch. Any bounce will be back to the 'unchanged' state.



See lecture notes for complete explanation.

For active high

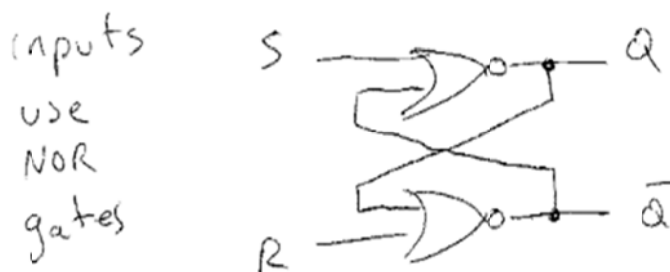

S	R	Q
0	0	unchanged
0	1	0
1	0	1
1	1	not allowed

2.


States

A \Rightarrow no 1's found (reset state)

B \Rightarrow first 1 found

C \Rightarrow two ones found

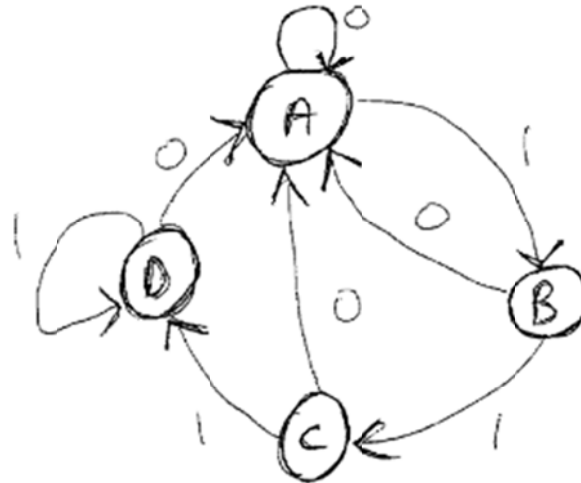D \Rightarrow three ones found (at least)




	Present state			Next state		
	Q_1	Q_0	I	Q_1'	Q_0'	Z
A	0	0	0	0	0	0
B	0	1	0	0	0	0
C	1	0	0	0	0	0
D	1	1	0	0	0	1

$$Z = Q_1 Q_0$$


$$\begin{aligned}
 Q_1' &= \bar{Q}_1 \bar{Q}_0 I + Q_1 \bar{Q}_0 I + Q_1 Q_0 I \\
 &= \bar{Q}_1 Q_0 I + Q_1 I \\
 &= (\bar{Q}_1 Q_0 + Q_1) I \\
 &= (Q_1 + Q_0) I *
 \end{aligned}$$
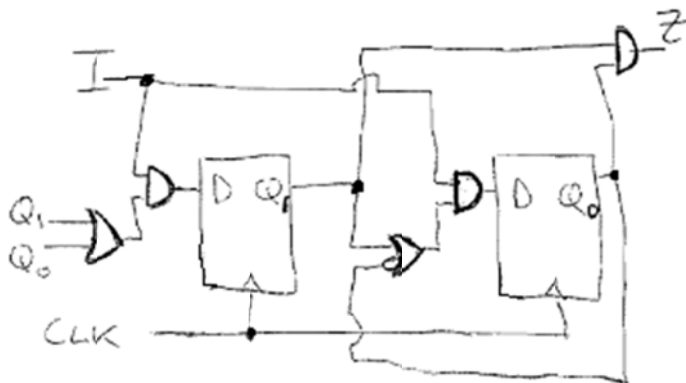
$$\begin{aligned}
 Q_0' &= \bar{Q}_1 \bar{Q}_0 I + Q_1 \bar{Q}_0 I + Q_1 Q_0 I \\
 &= \bar{Q}_1 \bar{Q}_0 I + Q_1 I (\bar{Q}_0 + Q_0) \\
 &= \bar{Q}_1 \bar{Q}_0 I + Q_1 I \\
 &= (\bar{Q}_1 \bar{Q}_0 + Q_1) I \\
 &= (Q_1 + \bar{Q}_0) I *
 \end{aligned}$$




* Final steps make use of simplification theorem.

3.

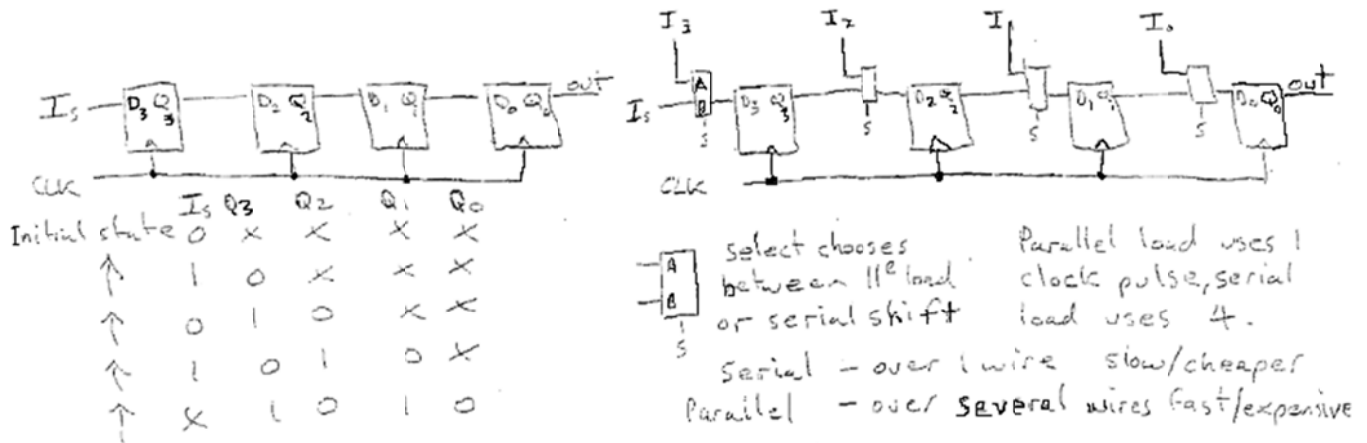

4.

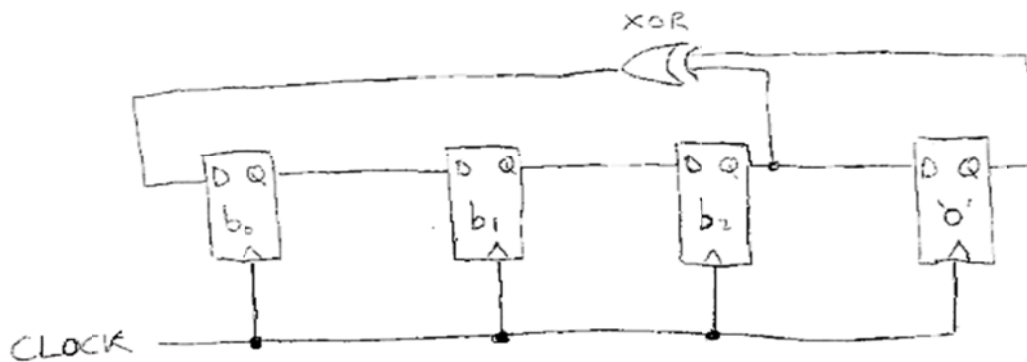

The rule for producing Gray Code tells us to copy down the MSB (same in Gray and Binary). The 'hint' tells you how to do this in the circuit. Load the register as shown initially.

	b_3	b_2	b_1	b_0
↑	g_3	b_3	b_2	b_1
↑	g_2	g_2	b_1	b_0
↑	g_1	g_1	g_1	b_0

Three clocks later, the binary has been replaced with Gray Code.

5.


Find '0100'

A no bits found

B first '0' found

C found '01'

D found '010'

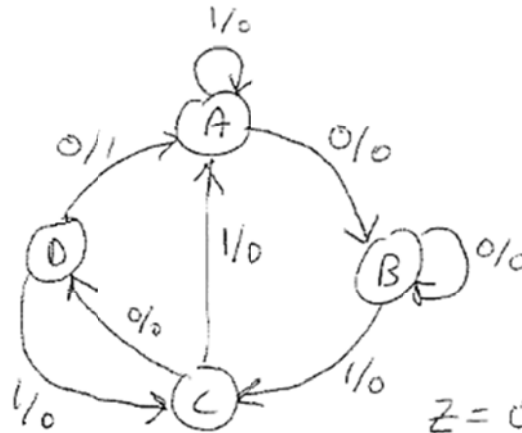

$$Z = Q_1 Q_0 \bar{I}$$

	Present State	Input I	NEXT STATE	OUTPUT
A	00	0	01	0
		1	00	0
B	01	0	01	0
		1	10	0
C	10	0	10	0
		1	00	1
D	11	0	00	0
		1	10	0

$$\begin{aligned}
 Q_1' &= \bar{Q}_1 \bar{Q}_0 \bar{I} + \bar{Q}_1 Q_0 \bar{I} + Q_1 \bar{Q}_0 \bar{I} \\
 &= \bar{Q}_1 \bar{I} + Q_1 \bar{Q}_0 \bar{I} \\
 &= \bar{I} (\bar{Q}_1 + Q_1 \bar{Q}_0) \\
 &= \bar{I} (\bar{Q}_1 + \bar{Q}_0) = \bar{I} \bar{Q}_1 + \bar{I} \bar{Q}_0 \\
 &\quad [\text{as } x + \bar{x}y = x + y]
 \end{aligned}$$

Several circuit solutions are possible depending on your simplification of the equations.

$$\begin{aligned}
 Q_1' &= \bar{Q}_1 \bar{Q}_0 \bar{I} + Q_1 \bar{Q}_0 \bar{I} + Q_1 Q_0 \bar{I} \\
 &= \bar{Q}_0 \bar{I} + Q_1 \bar{Q}_0 \bar{I}
 \end{aligned}$$

